



6-6

HDL for Registers and Counters

J.J. Shann

■124



HDL Models of Registers and Counters

- HDL models of registers and counters:
 - **Behavioral level:** describes only the operations of the register, as prescribed by a **function table**, w/o a preconceived structure.
 - **Structural level:** shows the ckt in terms of a collection of components such as **gates**, **flip-flops**, and **multiplexers**.
 - The various components are instantiated to form a **hierarchical** description of the design.
- * When a machine is complex, a **hierarchical** description creates a physical partition of the machine into simpler and more easily described units.



J.J. Shann HDL-125

■125

A. Shift Register

■ Universal shift register:

– p. 353, Fig 6.7, p.354, Table 6.3

 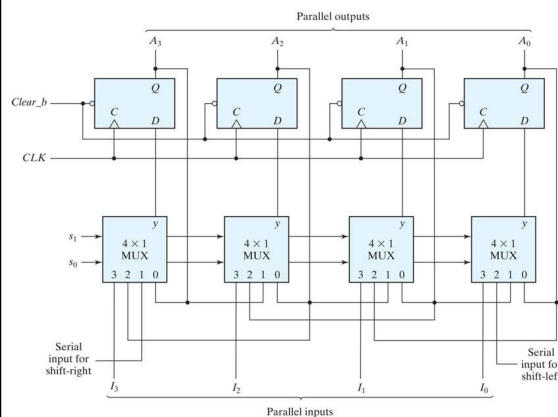

Function table


Mode Control		
s ₁	s ₀	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

J.J. Shann HDL-126

■126

HDL Example 6.1: Universal Shift Register (Behavioral Model)

 ■ HDL Example 6.1: 4-bit Universal Shift Register (Behavioral Model)-- p. 353, Fig 6.7(a), p.354, Table 6.3




Mode Control		
s ₁	s ₀	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load

```

module Shift_Register_4_beh (           // V2001, 2005
    output reg [3:0] A_par,             // Register output
    input [3:0] I_par,                  // Parallel input
    input s1, s0,                      // Select inputs
    input MSB_in, LSB_in,              // Serial inputs
    input CLK, Clear_b                  // Clock and Clear_b
);
    
```

-127

■127




```

module Shift_Register_4_beh (
  output reg [3:0] A_par,
  input [3:0] I_par,
  input s1, s0,
  input MSB_in, LSB_in,
  input CLK, Clear_b
);

  always @ (posedge CLK, negedge Clear_b)
    if (~Clear_b) A_par <= 4'b0000;
    else
      case ({s1, s0})
        2'b00: A_par <= A_par; // No change
        2'b01: A_par <= {MSB_in, A_par[3:1]}; // Shift right
        2'b10: A_par <= {A_par[2:0], LSB_in}; // Shift left
        2'b11: A_par <= I_par; // Parallel load of input
      endcase
endmodule

```

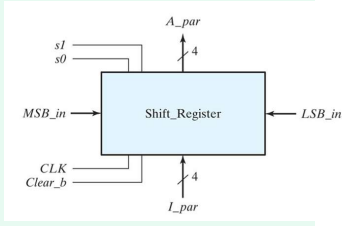

Mode Control		
s1	s0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


128

■128

HDL Example 6.2: Universal Shift Register (Structural Model)

■ HDL Example 6.2: 4-bit University Shift Register
(Structural Model)

— p. 353, Fig 6.7(a)(b)

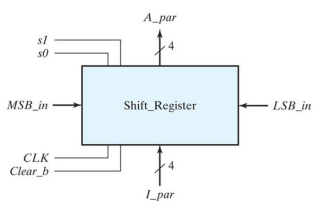

```


module Shift_Register_4_str (
  output [3:0] A_par,
  input [3:0] I_par,
  input s1, s0,
  input MSB_in, LSB_in, CLK, Clear_b
);

```


```

// V2001, 2005
// Parallel output
// Parallel input
// Mode select
// Serial inputs, clock, clear


```

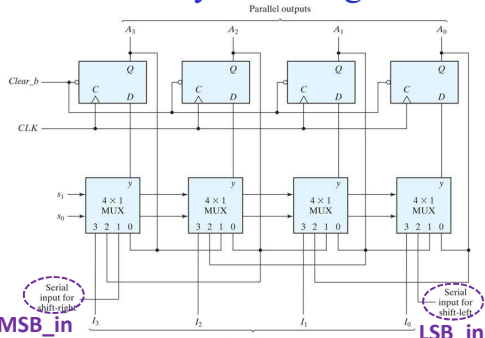

■129

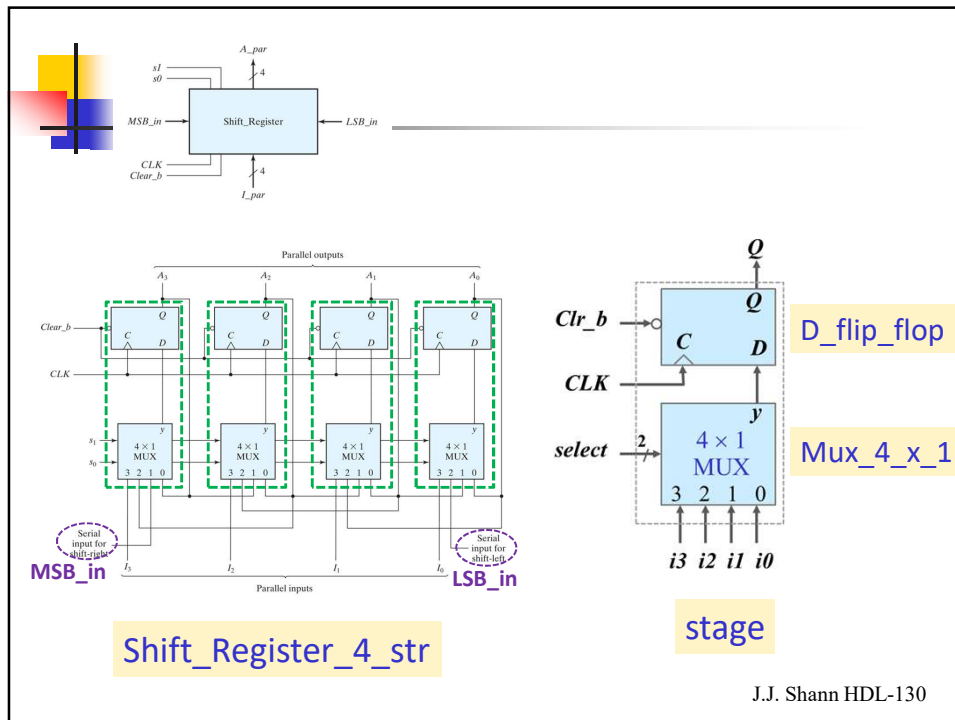

■130

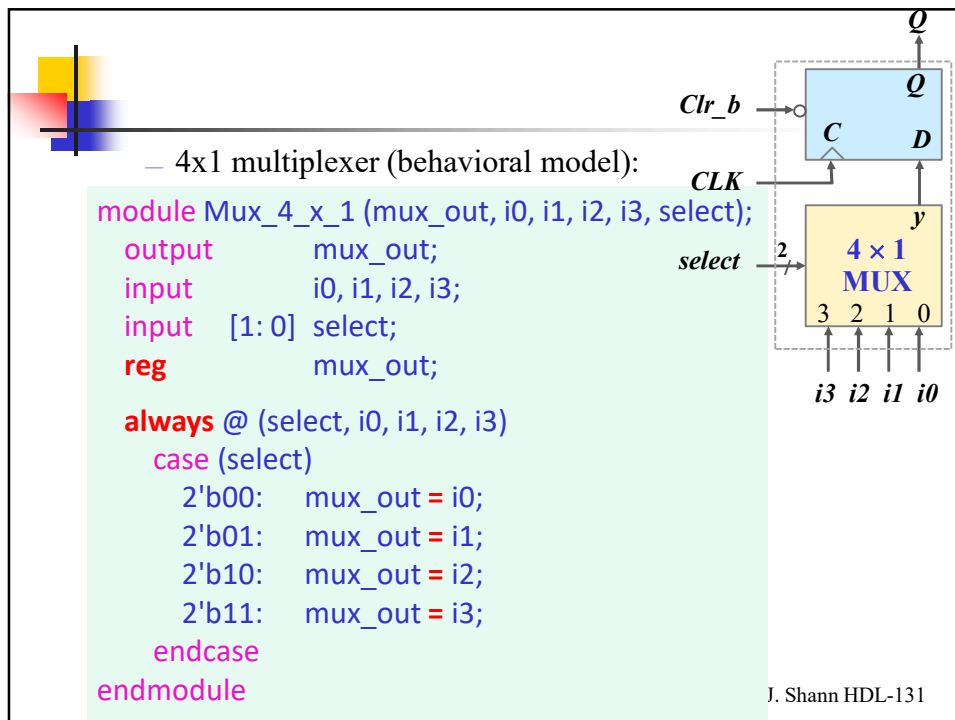

■131

– D flip-flop (behavioral model):

```

module D_flip_flop (Q, D, CLK, Clr_b);
  output Q;
  input D, CLK, Clr_b;
  reg Q;

  always @ (posedge CLK or negedge Clr_b)
    if (!Clr_b) Q <= 1'b0; else Q <= D;
endmodule

```

J.J. Shann HDL-132

■132

– 1-stage of shift register:

```


module stage (i0, i1, i2, i3, Q, select, CLK, Clr_b);
  input i0, //circulation bit selection
        i1, //data from left neighbor or serial input for shift-right
        i2, //data from right neighbor or serial input for shift-left
        i3; //data from parallel input

  output Q;
  input [1:0] select; //stage mode control bus
  input CLK, Clr_b; //Clock, Clear for flip-flops
  wire mux_out;


  // instantiate mux and flip-flop
  Mux_4_x_1 M0 (mux_out, i0, i1, i2, i3, select);
  D_flip_flop M1 (Q, mux_out, CLK, Clr_b);
endmodule

```

■133

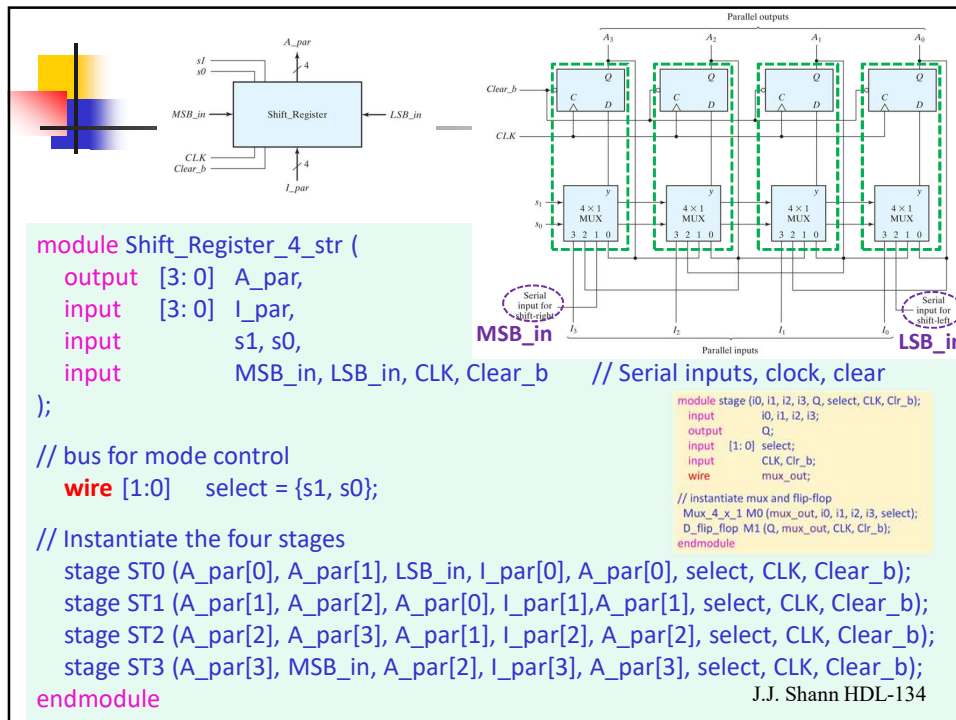


■134

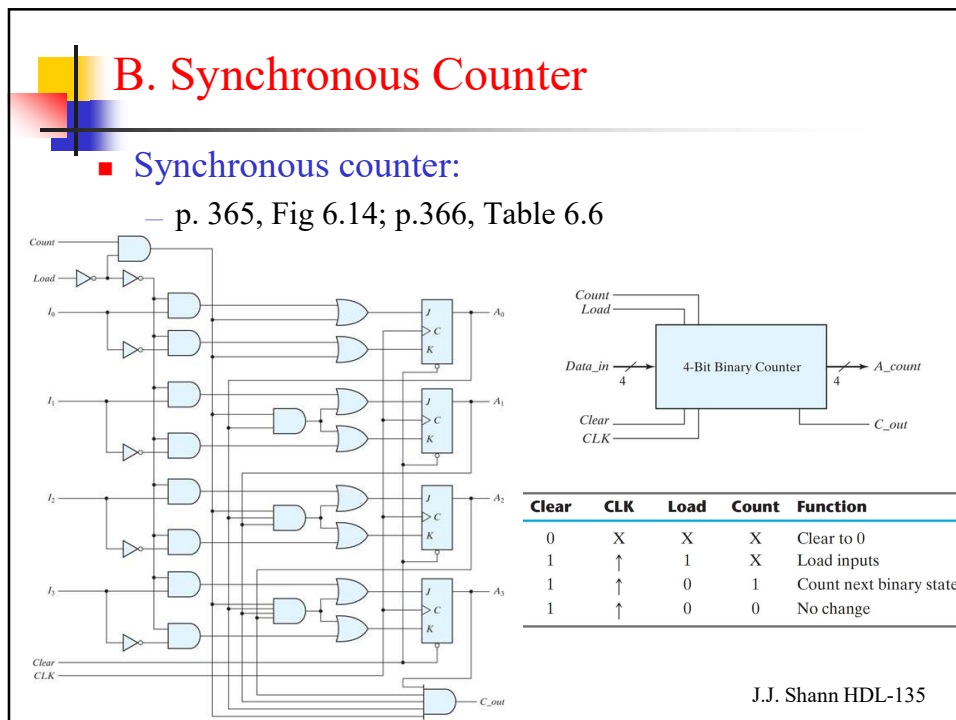

■135

HDL Example 6.3: Synchronous Counter

 ■ HDL Example 6.3: 4-bit Binary Counter with Parallel Load-- p.366, Table 6.6, p. 365, Fig 6.14



Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

```

module Binary_Counter_4_Par_Load (
    output reg [3:0] A_count, // Data output
    output          C_out,    // Output carry
    input [3:0]     Data_in,  // Data input
    input          Count,     // Active high to count
    input          Load,     // Active high to load
    input          CLK,       // Positive edge sensitive
    input          Clear_b    // Active low
);


```

■136

```

module Binary_Counter_4_Par_Load (
    output reg [3:0] A_count, // Data output
    output          C_out,    // Output carry
    input [3:0]     Data_in,  // Data input
    input          Count,     // Active high to count
    input          Load,     // Active high to load
    input          CLK,       // Positive edge sensitive
    input          Clear_b    // Active low
);
    assign C_out = Count & (~Load) & (A_count == 4'b1111);
    always @ (posedge CLK, negedge Clear_b)
        if (~Clear_b)    A_count <= 4'b0000;
        else if (Load)    A_count <= Data_in;
        else if (Count)   A_count <= A_count + 1'b1;
        else              A_count <= A_count; // redundant statement
endmodule

```

 


Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

■137

C. Ripple Counter

- Ripple counter:
 - p.356, Fig 6.8(b)

 

J.J. Shann HDL-138


■138

Summary of HDL

- HDLs are extremely important tools for modern digital designers.
- HDLs are used for both *simulation* and *synthesis*.
- **Writing HDL code \Rightarrow describing *real hardware*!**
 1. Sketch a *block diagram* of your system.
 2. Identify which portions are *combinational logic* and which portions are *sequential circuits or FSMs*.
 3. Write HDL code for each portion, using the correct idioms to imply the kind of hardware needed.

J.J. Shann 1-143

■143



Guidelines of Blocking and Nonblocking Assignments (p. HDL-94)

- Use *continuous assignments* **assign** to model *simple combinational* logic.
- Use **always @ (*)** and *blocking assignments* (=) to model more *complicated combinational* logic where the **always** statement is helpful.
- Use **always @ (posedge clk)** and *nonblocking assignments* (<=) to model *synchronous sequential* logic.
- Do not make assignments to the same signal in more than one **always** statement or continuous assignment statement.

J.J. Shann HDL-144