


# Chapter 7

---

## Memory & Programmable Logic


*J.J. Shann*

1




### Contents

---

7-1	Introduction	
7-2	Random-Access Memory (RAM)	
7-3	Memory Decoding	
7-4	Error Detection and Correction	
7-5	Read-Only Memory (ROM)	
7-6	Programmable Logic Array (PLA)	
7-7	Programmable Array Logic (PAL)	
7-8	Sequential Programmable Devices	

*J.J. Shann 7-2*

2

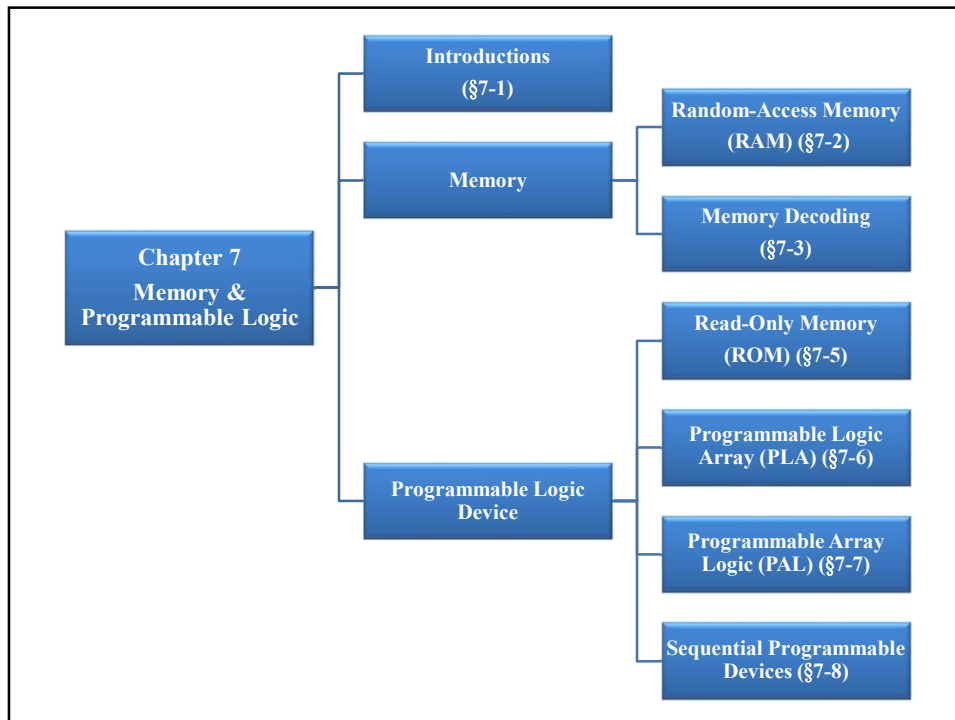

3


## Exercises in Textbook (6<sup>th</sup> ed)

Sections	Exercises	Typical Ones
§7-2	7.1~7.4	7.1(a), 7.2(a)
§7-3	7.6~7.9, 7.15, 7.16	7.6, 7.7*, 15
§7-4	7.10~7.14	7.11
§7-5	7.17, 7.18, 7.20, 7.22	7.18(b)
§7-6	7.19, 7.21, 7.23, 7.28, 7.29	7.19
§7-7	7.24, 7.25	7.25*
§7-8	7.26, 7.27	7.26
HDL	7.5, 7.30	

\* : Answers to problems appear at the end of the text.

J.J. Shann 7-4

4




7-1

---

Introduction

J.J. Shann


5



Introduction

---

Digital computer:

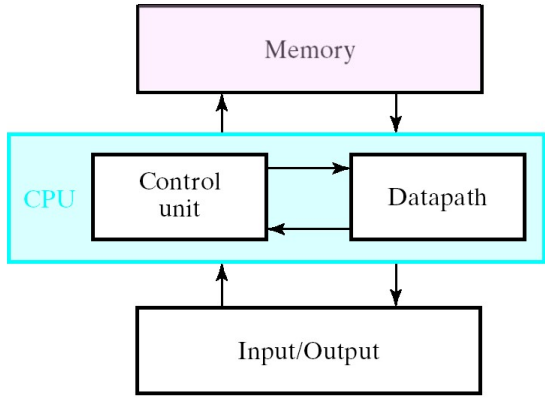

```
graph TD; Memory[Memory] <--> CPU; subgraph CPU; direction LR; CU[Control unit] <--> DP[Datapath]; end; IO[Input/Output] <--> CPU;
```

J.J. Shann 7-6


6

## Memory Unit

### ■ Memory unit:

- is a device to which binary information is transferred for storage and from which information is available when needed for processing
- Binary storage cells + Associated circuits for storing and retrieving the information.
- Operations: *Write* & *Read* operations
- Two types of memories used in digital systems:
  1. **RAM**: Random-access memory (*Write* & *Read* ops)
    - Stores data temporarily.
    - Applications: Cache, main memory (SRAM) (DRAM)
  2. **ROM**: Read-only memory (only *Read* op) ⇒ PLD
    - Stores data permanently: a suitable binary information is already stored inside the memory.

J.J. Shann 7-7

 

7


## Programmable Logic Device

### ■ Programmable logic device (PLD):

- is an IC w/ internal **logic gates** that are connected through **electronic paths** that behave similar to fuses.
  - In the original state of the device, all the fuses are intact.
  - Programming the device:
    - blow those fuses along the paths that must be removed in order to obtain the particular configuration of the desired logic function.
- ⇒ a hardware procedure that specifies the bits that are inserted into the hardware configuration of the device
- E.g.s of PLD:
  - ROM, PLA, PAL, FPGA
  - FPGA: Field-programmable gate array


J.J. Shann 7-8

8




---

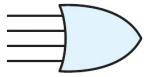
■ Conventional & Array logic diagrams for OR gate:



(a) Conventional symbol

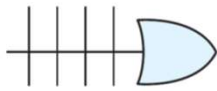


(b) Array logic symbol



J.J. Shann 7-9

9



---

**7-2**

**Random-access  
Memory**

*J.J. Shann*

10

## Random-access Memory

### ■ Memory unit:

- a collection of *storage cells* together w/ *associated ckt*s needed to transfer information in and out of the device
- *word*: an entity of bits that move in & out of storage as a unit
- *capacity* of a memory unit: # of bytes it can store  
# words, # bits/word


### ■ Random-access memory :

- the time it takes to transfer information to or from any desired random location is always the same

J.J. Shann 7-11

11

### ■ Block diagram of a memory unit:

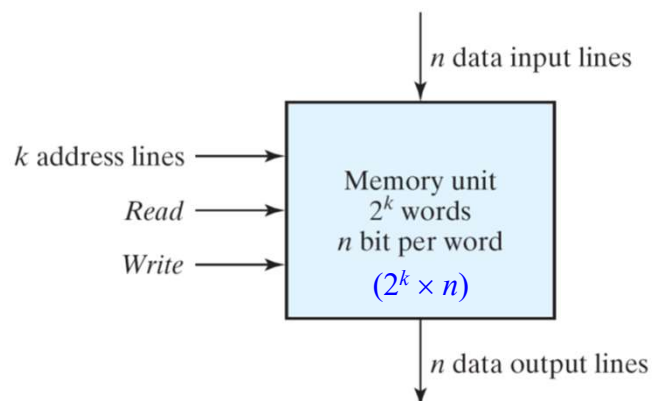

J.J. Shann 7-12

12

- Example: a  $1024 \times 16$  memory  $\Rightarrow 2^{10} \times 16$

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

J.J. Shann 7-13


13

## A. Write & Read Operations

- *Write op: transfer-in*

— Steps:

 - Apply the binary **addr** of the desired word to the addr lines.
- Apply the **data** bits that must be stored in memory to the data input lines.
- Activate the **Write** input.




- *Read op: transfer-out*

— Steps:

- Apply the binary **addr** of the desired word to the addr lines.
- Activate the **read** input.

J.J. Shann 7-14

14




■ **Control inputs to a RAM chip:**

- *Read* signal, *Write* signal
- *Memory enable (Chip Select)*, *Read/Write*

**Control Inputs to Memory Chip**

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

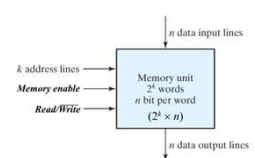

J.J. Shann 7-15

15

## B. Memory Description in HDL

■ Memory is modeled in the Verilog HDL by an array of registers:

- is declared with a **reg** keyword, using a *two-dimensional array*
- E.g.: a memory of 1024 words with 16 bits/word  
 ⇒ a 2D array of 1024 registers, each containing 16 bits

```
reg [15:0] memword [0:1023];
```

# of bits in a word (*word length*)      # of words in memory (*memory depth*)

\* memword[512] refers to the 16-bit memory word at address 512.


J.J. Shann 7-16

16


 
## HDL Example 7.1: Operation of a Memory Unit

- HDL Example 7.1: Read and write operations of a memory with 64 words of 4 bits each



**\* The memory has three-state outputs.**

Enable	ReadWrite	Memory operation
0	x	None ( $\text{DataOut} \leftarrow \text{Hi-Z}$ )
1	0	Write to selected word ( $\text{Mem}[\text{Address}] \leftarrow \text{DataIn}$ )
1	1	Read from selected word ( $\text{DataOut} \leftarrow \text{Mem}[\text{Address}]$ )

17

Enable	ReadWrite	Memory operation
0	x	DataOut $\leftarrow$ Hi-Z
1	0	Mem[Address] $\leftarrow$ DataIn
1	1	DataOut $\leftarrow$ Mem[Address]

```

module memory (Enable, ReadWrite, Address, DataIn, DataOut);
    input      Enable, ReadWrite;
    input  [3: 0] DataIn;
    input  [5: 0] Address;
    output [3:0] DataOut;
    reg    [3: 0] DataOut;
    reg    [3: 0] Mem [0: 63];           //64 x 4 memory
    always @ (Enable or ReadWrite)
        if (Enable)
            if (ReadWrite) DataOut = Mem[Address]; //Read
            else Mem[Address] = DataIn;           //Write
            else DataOut = 4'bz;                  //High impedance state
endmodule
    
```

18

## C. Timing Waveforms


### ■ Operation of a memory unit:

- is controlled by an external device such as a CPU.
  - The CPU is usually synchronized by its own clock.
  - The memory does not employ an internal clock.
- Its read & write operations are specified by control inputs.
- ⇒ The CPU must provide the memory control signals to synchronize its internal clocked operations w/ the read and write operations of memory.

### ■ Access time: (\*)

- **read cycle time**: the max time from the application of the addr to the appearance of the data at the Data Output
- **write cycle time**: the max time from the application of the addr to the completion of all internal memory ops required to store a word
- The access time of the memory must be related within the CPU to a period equal to a fixed # of CPU clock cycles.

J.J. Shann 7-19

 


19

### ■ Example: CPU – 50MHz clock frequency (20 ns)


Memory – access time & cycle time does not exceed 50 ns

#### Write cycle

 

J.J. Shann 7-20

20

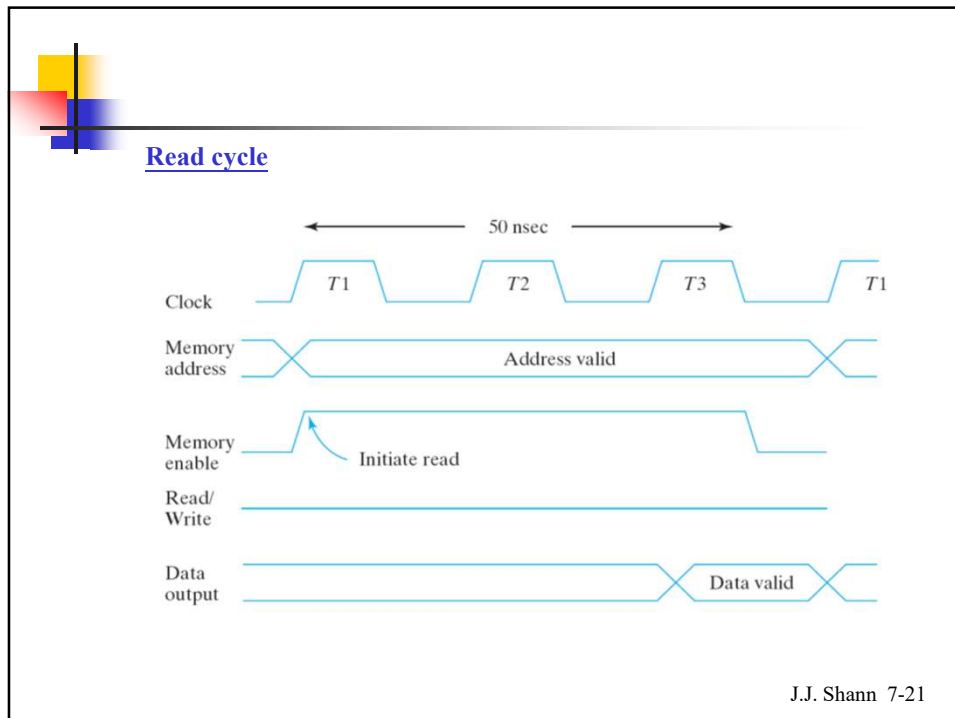


21

## D. Types of Memory

- Random-access vs. Sequential-access memory:
  - Sequential-access memory: magnetic disk or tape unit
- Operating modes of RAMs:
  1. Static RAM: SRAM (Cache)
    - Consists essentially of internal **latches** that store the binary information.
    - The stored information remains valid as long as power is applied to the RAM.
  2. Dynamic RAM: DRAM (Main memory)
    - Stores the binary information in the form of electric charges on **capacitors**.
    - The stored information remains valid as long as power is applied to the RAM.

J.J. Shann 7-22

22




---

- **Volatile vs. Nonvolatile memory:**
  - Volatile:
    - Lose stored information when power is turned off.
    - E.g.: static & dynamic RAMs
  - Nonvolatile:
    - Retains its stored information after the removal of power
    - E.g.: magnetic disk, ROM

J.J. Shann 7-23

23



---

- **Memory used in digital computers:**
  - Programs and data that cannot be altered are stored in **ROM**.

Other large programs are maintained on **magnetic disks**.
  - When power is turned on, the computer can use the programs from **ROM**.

The other programs residing on a **magnetic disk** are then transferred into the computer **RAM** as needed.

Before turning the power off, the binary information from the computer **RAM** is transferred into the **disk** for the information to be retained.

J.J. Shann 7-24

24

## E. Memory Cells of RAM (§7-3 + 補充資料)

### ■ Types of RAMs:


1. **Static RAM (SRAM):** Volatile → **Cache**
  - Consists essentially of internal **latches** that store the binary information.
  - Advs.: easier to use, shorter read and write cycles, & no refreshing
2. **Dynamic RAM (DRAM):** Volatile → **Main memory**
  - Stores the binary information in the form of electric charges on **capacitors**.
  - The capacitors must be periodically recharged by **refreshing** the DRAM (every few milliseconds).
  - Advs.: reduced power consumption & larger storage capacity

J.J. Shann 7-25

25

## SRAM Cell (§7-3)
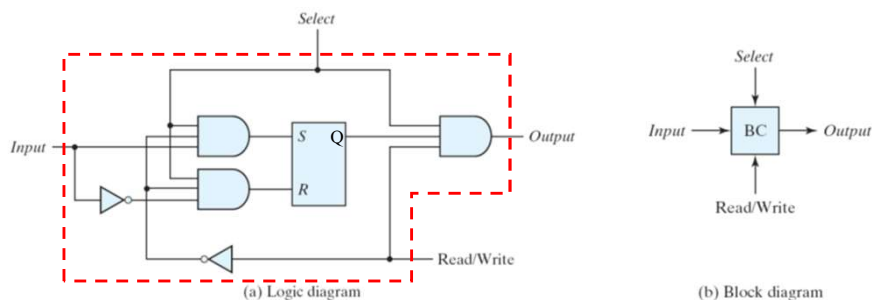
### ■ SRAM memory cell: stores one bit of information



Select	Read/Write	S	R	$Q^+$	Output
0	×	0	0	Q	0
1	0	Input	Input'	Input	0
1	1	0	0	Q	Q


26

(Supplementary Materials)

## 補充資料：DRAM Cell


### ■ SRAM cell vs. DRAM cell:

#### SRAM cell

 

- 6 transistors

#### DRAM cell



 


- 1 transistor (T) & 1 capacitor (C)
- Leaks  $\Rightarrow$  Refresh
- Destructive read  $\Rightarrow$  Restore


J.J. Shann 7-27

27


### ■ Hydraulic analogy of DRAM cell op:

   

Write op:

 

 
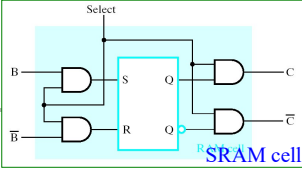
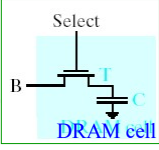
Read op:  
(destructive read)



J.J. Shann 7-28

28



■ **Advs. of DRAM:**

- Density: have 4 times the density of SRAM.
- Cost/bit: is 3 to 4 times less than SRAM.
- Power: lower power requirement


⇒ DRAM is the preferred technology for large memories (e.g.: main memory).

■ **Disadv. of DRAM:**

- its electronic design is considerably more challenging:
  - Destructive read ⇒ Restore
  - Leaks ⇒ Refresh

J.J. Shann 7-29

29



7-3

---


## Memory Decoding

*J.J. Shann*

30
 
## Memory Decoding

- Memory unit: storage components + decoding ckts
  - Decoding ckts: select the memory word specified by the input address
- RAM of  $m$  words &  $n$  bits/word:
  - $m \times n$  binary storage cells + associated decoding ckts




J.J. Shann 7-31

31
 
## A. Internal Construction


- Logical construction of a RAM:  $2^k$  words  $\times$   $n$  bits/word
  - $2^k \times n$  binary storage cells + associated decoding ckts
  - Decoding ckts: *Linear decoding*
    - Requires  $k$  address lines that go into a  $k \times 2^k$  decoder
    - Each one of the decoder outputs selects one word of  $n$  bits for reading or writing.



J.J. Shann 7-32

32



 

33

## B. Coincident decoding

- Linear decoding:  $2^k$  words
  - Employ a  $k \times 2^k$  decoder
- Coincident decoding:  $2^k$  words
  - 2-D coincident decoding:
    - Employ two decoders in a **two-dimensional selection** scheme  
 ⇒ **two  $k/2$ -input decoders** (row selection & column selection)
    - \* Notice: arrange the memory cells in an array that is as close as possible to **square**

	<u>Linear</u>	<u>Coincident (2D)</u>
Decoder	1 $k \times 2^k$	2 $k/2 \times 2^{k/2}$
# AND gates	$2^k$	$2 \times 2^{k/2} (= 2^{k/2+1})$
# inputs/gates	$k$	$k/2$
Read & write times	longer	shorter

Assumption:  $k$  is an even number


J.J. Shann 7-34

34

## Example

- Example: a 1K-word memory  $\Rightarrow$  10 address lines

### Linear decoding:

 


J.J. Shann 7-35

35

a 1K-word memory  $\Rightarrow$  10 address lines

### 2-D coincident decoding:

 

J.J. Shann 7-36

36

■ The savings of the coincident selection scheme:

- A single 10-to-1024 decoder:
  - 1024 AND gates w/ 10 inputs in each
- Coincident selection: two 5-to-32 decoders
  - $2 \times (32 \text{ AND gates w/ } 5 \text{ inputs in each})$
  - $\Rightarrow 64 \text{ AND gates w/ } 5 \text{ inputs in each}$

	<u>Linear</u>	<u>Coincident (2D)</u>
Decoder	1 $k \times 2^k$	2 $k/2 \times 2^{k/2}$
# AND gates	$2^k$	$2 \times 2^{k/2} (= 2^{k/2+1})$
# inputs/gates	$k$	$k/2$
Read & write times	longer	shorter

J.J. Shann 7-37


37

**Example**

\* Arrange the memory cells in an array that is as close as possible to **square**.

■ E.g.: For a 32K×8 RAM

 - Linear selection scheme:
  - A single 15-to- $2^{15}$  line decoder:
    - $\Rightarrow 32,768 \text{ AND gates w/ } 15 \text{ inputs in each}$



- Coincident selection:
  - Make the # of rows and columns in the array equal:
    - (\*Arrange the memory cells in the array as close to square as possible.)
    - $32K \times 8 = 256K \text{ bits} = 2^{18} \text{ bits} = 2^9 \times 2^9$
    - $= 2^9 \times (2^6 \times 8) \text{ bits}$
    - row selection      column selection
    - $\Rightarrow$  a 9-to-512 line decoder (row) & a 6-to-64 line decoder (column)
    - $\Rightarrow 512 \text{ 9-input AND gates \& } 64 \text{ 6-input AND gates}$
    - $\Rightarrow 576 \text{ AND gates (with 9- or 6-input in each)}$



J.J. Shann 7-38

38

## C. Address Multiplexing

### ■ Address multiplexing:


- Reduce the # of pins in the IC package
- Use one set of address input pins accommodates the address components.
- E.g.: In a 2-dimensional array, the same set of pins is used for both of the row and column addresses

J.J. Shann 7-39

39

## Example
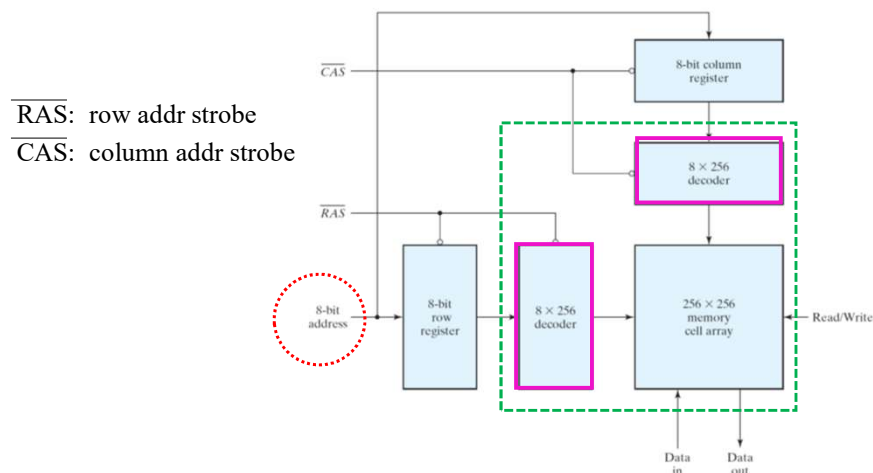
### ■ Example: a 64K DRAM ( $64K = 2^{16}$ )



J.J. Shann /-40

40

(Supplementary Materials)


## 補充資料：Array of SRAM ICs

### ■ Memory unit:

– Capacity: # words, # bits/word

### ■ Symbol for a RAM chip:

– E.g.: 64K × 8 RAM

 

J.J. Shann 7-41

41

## Increasing # of Words

### ■ E.g.:

Construct a 256K×8 RAM  
by using 64K×8 RAM ICs


$(2^{18})$

256K×8 RAM



four 64K×8 RAM ICs

$(2^{16})$

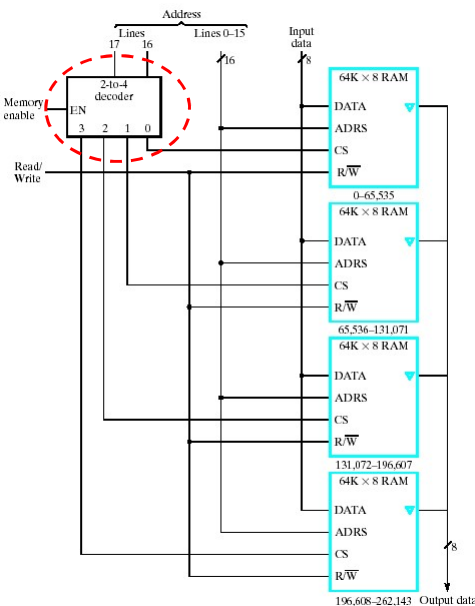


42

## Increasing # Bits/Word in the Memory
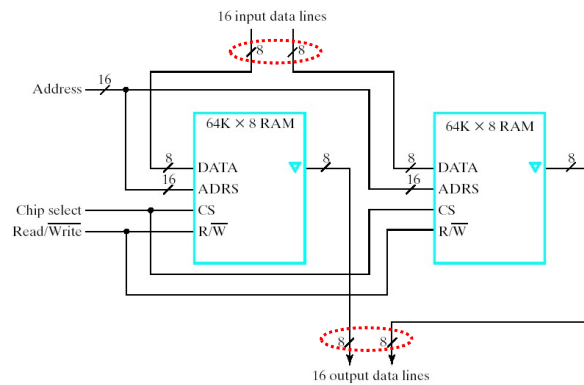
### E.g.:

Construct a 64K×16 RAM by using 64K×8 RAM ICs

64K×16 RAM  $\Rightarrow$  **two** 64K×8 RAM ICs



\* Increasing both # words & # bits/word?

J.J. Shann 7-43

43

## 7-5 ~ 7-7 Combinational PLDs

### Combinational PLD:


- is an IC w/ *programmable gates* divided into an **AND array** and an **OR array** to provide an **AND-OR sum of product** implementation.

### 3 major types of combinational PLDs:

- Differ in the placement of the **programmable connections** in the AND-OR array.
- 1. **PROM**: programmable read-only memory (§7-5)
- 2. **PAL**: programmable array logic (§7-7)
- 3. **PLA**: programmable logic array (§7-6)

J.J. Shann 7-56

56

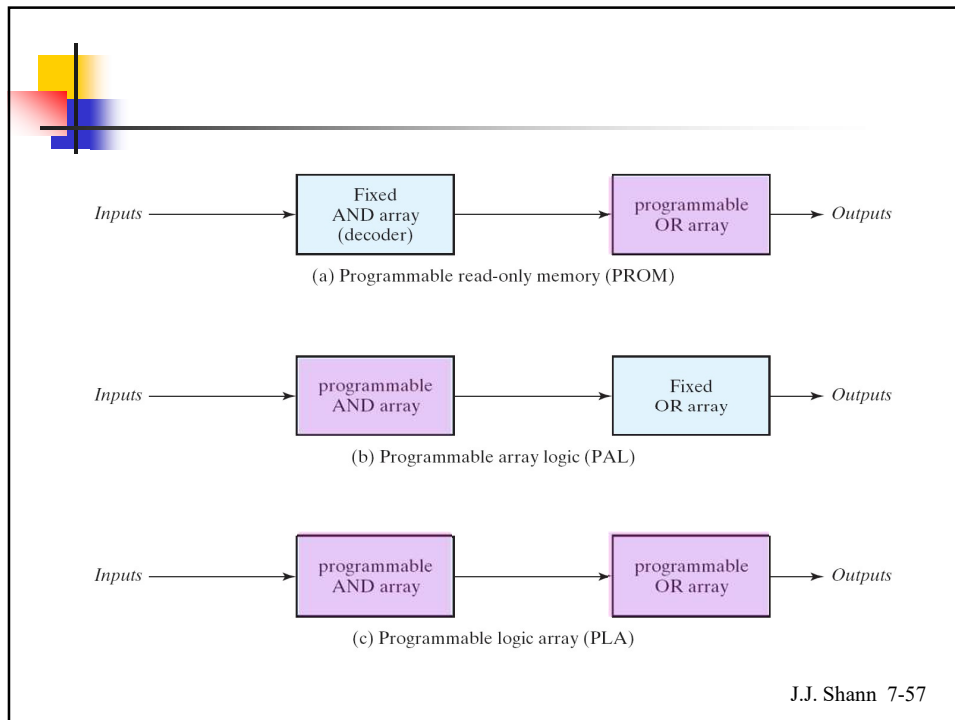

57

# 7-5

## Read-Only Memory (ROM)

J.J. Shann

58

# Read-Only Memory (ROM)

- ROM:
  - A memory device in which permanent binary information is stored

(a) Programmable read-only memory (PROM)

- ROM Block diagram:
 

$2^k \times n$  ROM

$2^k$  words,  $n$  bits/word

J.J. Shann 7-59

59

(a) Programmable read-only memory (PROM)  $2^k \times n$  ROM

- Internal logic of a  $2^k \times n$  ROM: comb. ckt.
  - have an internal  $k \times 2^k$  decoder &  $n$  OR gates
  - E.g.: a  $32 \times 8$  ROM


**programmable word**


(a) Conventional symbol (b) Array logic symbol

7-60

60





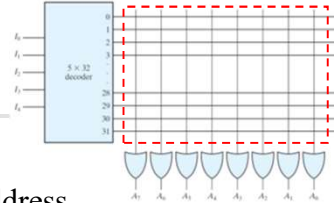

■ **ROM truth table:**


- shows the word content in each address
- gives all the information for programming the ROM
- E.g.:


*ROM Truth Table (Partial)*

Inputs					Outputs							
$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
			⋮						⋮			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

61

61



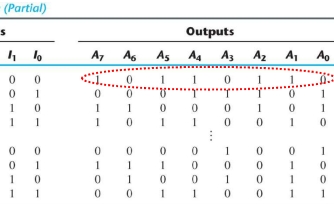

■ **Programming the ROM:**

- E.g.: Table 7-3 ⇒ Figure 7-11

*ROM Truth Table (Partial)*

Inputs					Outputs							
$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	0	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
			⋮						⋮			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	0	1	1	0	0	1

7-62

62

## Combinational Circuit Implementation

### ■ ROM: a decoder + OR gates

- Boolean functions → “**sum of minterms**” form
  - ROM truth table
  - ROM implementation
- For an  $n$ -input,  $m$ -output combinational ckt
  - ⇒  $2^n \times m$  ROM


### ■ Design procedure:

1. Determine the **size of ROM** required from the # of inputs and outputs of the comb. ckt.
2. Obtain the programming **truth table** of the ROM.
3. The 0's (or 1's) in the output functions of the truth table directly specify those links that must be removed to provide the required comb ckt in sum of minterms form.

J.J. Shann 7-63

63

## Example 7-1

 

### ■ E.g.: Design a combinational ckt using a ROM.

The ckt accepts a 3-bit number and generates an output binary number equal to the square of the input number.

<Ans.>

Truth table:

3 inputs & 6 outputs  
 ⇒  $2^3 \times 6$  ROM  
 ⇒ 8 words, 6 bits/word


Inputs			Outputs						Decimal
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

$B_1 = 0$

$B_0 = A_0$

J.J. Shann 7-64

64




### ROM implementation:

$B_1 = 0, B_0 = A_0$

Truth table (Table 7-4)  $\Rightarrow$  3 inputs, 4 outputs

$\Rightarrow$  a  $8 \times 4$  ROM

Inputs			Outputs						Decimal
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	0	1	0	4
0	1	1	0	0	0	1	0	0	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	0	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	1	0	0	0	49

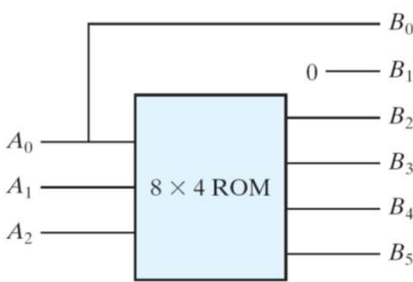


(a) Block diagram

$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0


(b) ROM truth table

J.J. Shann 7-65

65



## Types of ROMs



■ **Types of ROM:**

- Mask programming
- PROM: programmable ROM
- EPROM: erasable PROM
- EEPROM: electrically-erasable PROM

J.J. Shann 7-66

66

7-6

## Programmable Logic Array

J.J. Shann

67

### Programmable Logic Array

■ PLA:




(c) Programmable logic array (PLA)


- The array of AND gates can be programmed to generate any **product terms** (AND terms) of the input variables.
- The product terms are then connected to OR gates to provide the **sum of products** for the required Boolean functions.
- \* Compare to ROM:
  - does not provide full decoding of the variables
  - ⇒ does not generate all the minterms

J.J. Shann 7-68

68

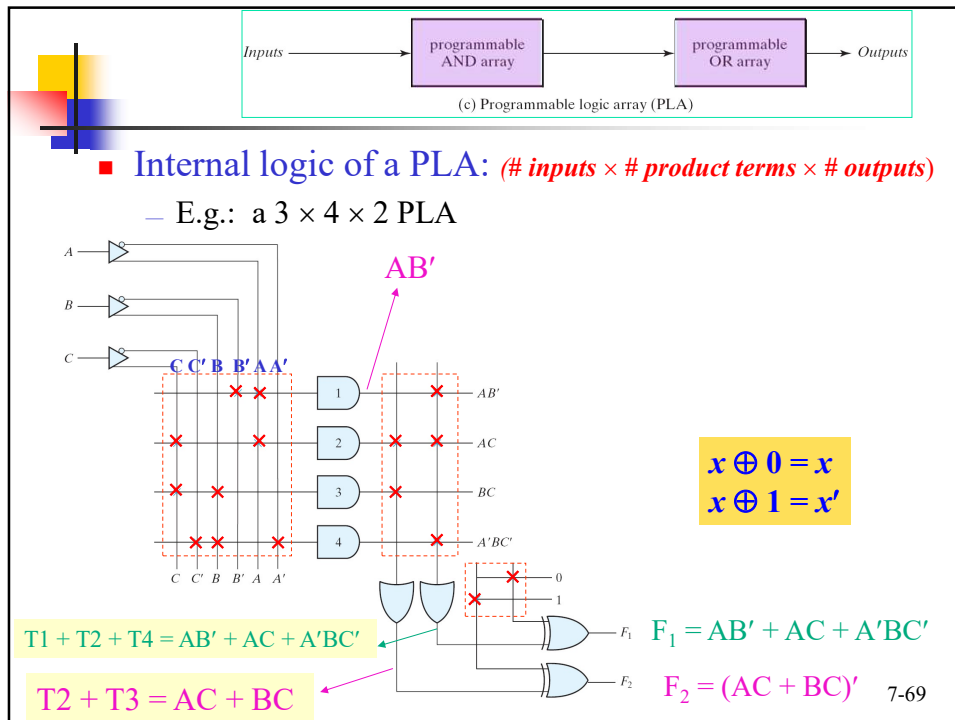

69

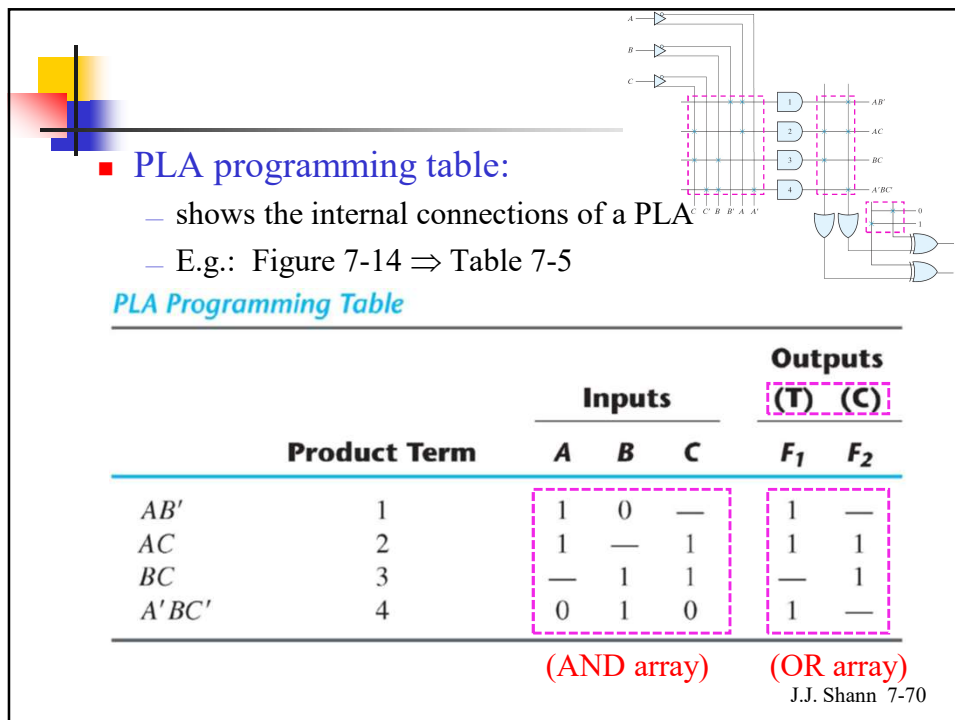


70

## Comb Ckt Implementation
 
### ■ Design method:

- **Sum-of-products form**
- A PLA has a finite # of AND gates  
 $\Rightarrow$  Reduce the # of **distinct product terms**.
- Both the **true** and **complement** of each function should be simplified to see which one can be expressed w/ fewer product terms and which one provides product terms that are common to other functions.  
 (\* The # of literals in a term is not important.)



J.J. Shann 7-71

71

## Example 7-2

- E.g.: Implement the following two Boolean functions w/ a PLA:

$$F_1(A, B, C) = \Sigma (0, 1, 2, 4)$$


$$F_2(A, B, C) = \Sigma (0, 5, 6, 7)$$

<Ans.>


		B			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0
		C			
		$F_1 = \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C}$			
		$\overline{F}_1 = AB + AC + BC$			

		B			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1
		C			
		$F_2 = AB + AC + \overline{A}\overline{B}\overline{C}$			
		$\overline{F}_2 = \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C}$			

72


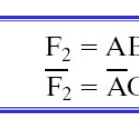
$$\begin{aligned} F_1 &= \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C} \\ \overline{F}_1 &= AB + AC + BC \end{aligned}$$



$$\begin{aligned} F_2 &= AB + AC + \overline{A}\overline{B}\overline{C} \\ \overline{F}_2 &= \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C} \end{aligned}$$

$$F_1 = A'B' + A'C' + B'C' \quad \begin{matrix} (6) \\ (4) \end{matrix} \quad F_2 = \overline{AB} + \overline{AC} + A'B'C'$$


$$F_1 = (\overline{AB} + \overline{AC} + \overline{BC})' \quad \begin{matrix} (6) \\ (6) \end{matrix} \quad F_2 = (A'C + A'B + AB'C')'$$

PLA programming table


		Inputs A B C			Outputs	
					(C) F <sub>1</sub>	(T) F <sub>2</sub>
AB	1	1	1	1	1	
AC	2	1	1	1	1	
BC	3	1	1	1	1	
$\overline{A}\overline{B}\overline{C}$	4	0	0	0	1	

J.J. Shann 7-73

73



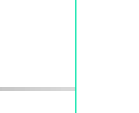
$$\begin{aligned} F_1 &= (\overline{AB} + \overline{AC} + \overline{BC})' \\ F_2 &= AB + AC + A'B'C' \end{aligned}$$



PLA programming table

		Inputs A B C			Outputs	
					(C) F <sub>1</sub>	(T) F <sub>2</sub>
AB	1	1	1	1	1	
AC	2	1	1	1	1	
BC	3	1	1	1	1	
$\overline{A}\overline{B}\overline{C}$	4	0	0	0	1	

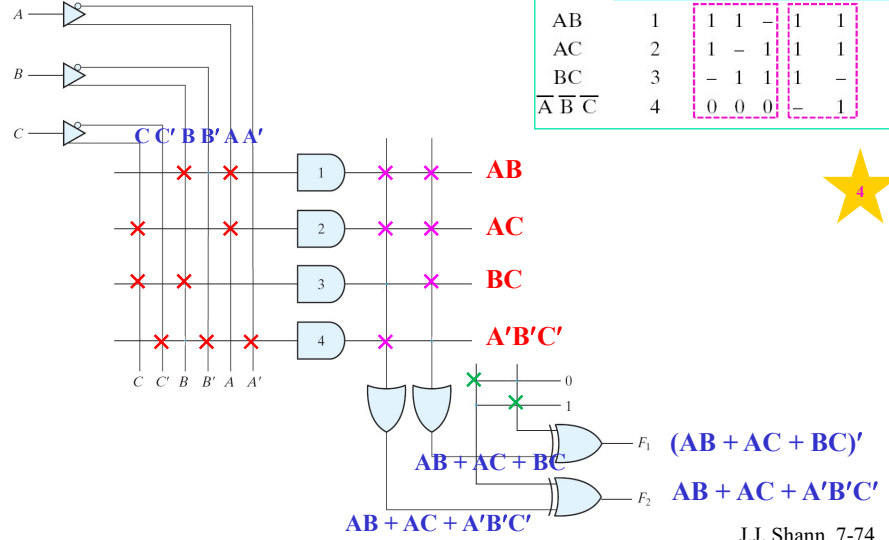

J.J. Shann 7-74

74

7-7


## Programmable Array Logic

*J.J. Shann*

75

## Programmable Array Logic

■ PAL:

 


(b) Programmable array logic (PAL)

- Only the AND gates are programmable.
- The PAL is easier to program, but is not as flexible as the PLA.

J.J. Shann 7-76


76



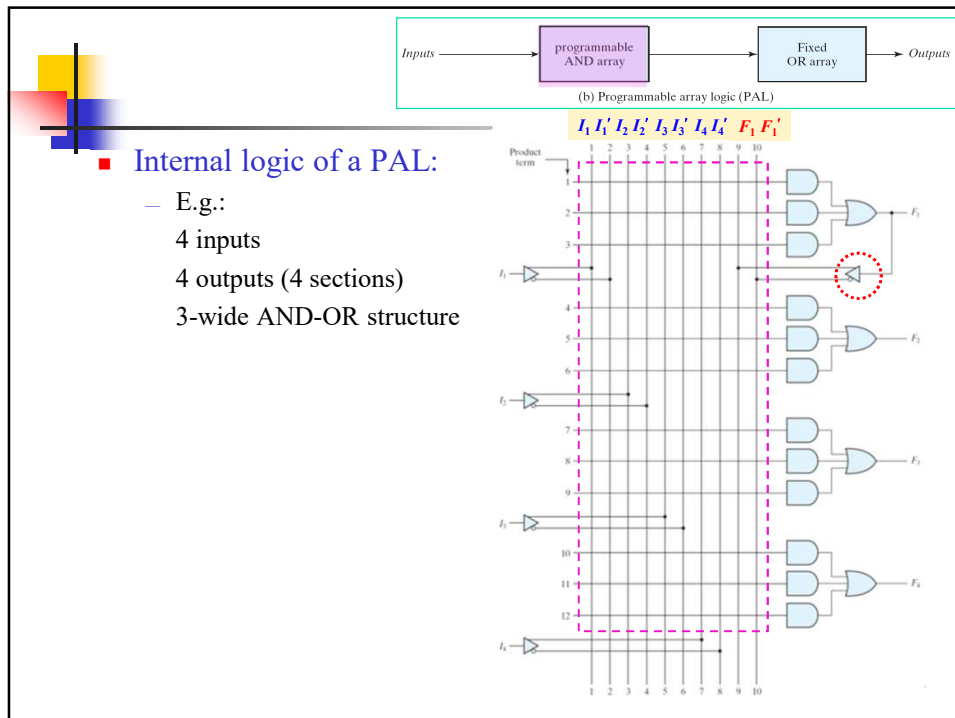
 
## Combination Circuit Implementation

- Design method:
  - The Boolean functions must be simplified to fit into each section.
  - Each function can be simplified by itself.(No sharing of product terms)
- If the # of terms in a function is too large, it may be necessary to use two sections to implement the function.
- PAL programming table



## Example

- Implement the following Boolean functions w/ a PAL:

$$w(A,B,C,D) = \Sigma(2,12,13)$$

$$x(A,B,C,D) = \Sigma(7,8,9,10,11,12,13,14)$$

$$y(A,B,C,D) = \Sigma(0,2,3,4,5,6,7,8,10,11,15)$$

$$z(A,B,C,D) = \Sigma(1,2,8,12,13)$$

<Ans.>


$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = \underline{ABC' + A'B'CD'} + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

 


J.J. Shann 7-79

79


PAL programming table

Product term	AND Inputs				W	Outputs
	A	B	C	D		
1	1	1	0	—	—	$W = ABC' + A'B'CD'$
2	0	0	1	0	—	
3	—	—	—	—	—	
4	1	—	—	—	—	$X = A + BCD$
5	—	1	1	1	—	
6	—	—	—	—	—	
7	0	1	—	—	—	$Y = A'B + CD + B'D'$
8	—	—	1	1	—	
9	—	0	—	0	—	
10	—	—	—	—	1	$Z = W + AC'D' + A'B'C'D$
11	1	—	0	0	—	
12	0	0	0	1	—	

 

J.J. Shann 7-80

80

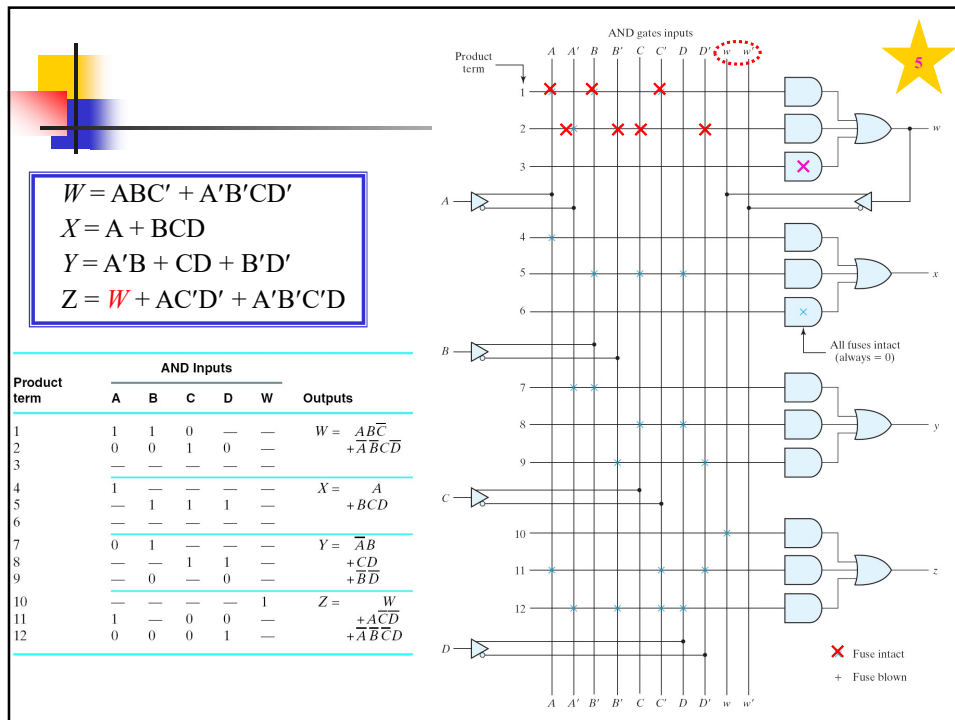

81

# 7-8

## Sequential Programmable Devices

*J.J. Shann*

82

## Sequential Programmable Devices

- Combinational PLD: (§7-5 ~ 7-7)
  - Consists of only **gates**
- Sequential PLD:
  - Include both **gates** & **flip-flops**
  - The device can be programmed to perform a variety of **sequential-ckt** functions
- Three major types of sequential PLD:
  - SPLD: Sequential (or simple) PLD
  - CPLD: Complex PLD
  - FPGA: Field programmable gate array


⇒ Require extensive CAD tools for their synthesis procedure.

J.J. Shann 7-83

83

 
## A. SPLD

- Sequential (simple) programmable logic device:
  - a PAL (or PLA) + a number of flip-flops




J.J. Shann 7-84

84



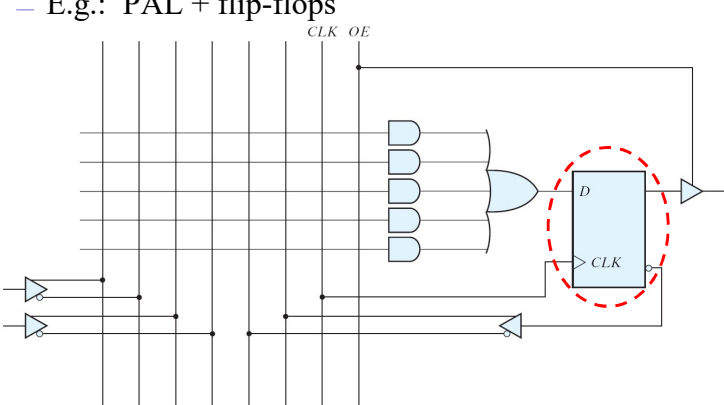
## Macrocell: a section of an SPLD

- Contains any one of the two-level comb logic function & an optional flip-flop
- E.g.: PAL + flip-flops




n 7-85

85


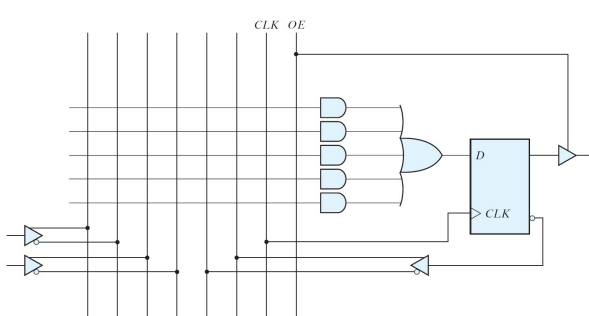
## Programming features:

- AND array
- ability to either use or bypass the flip-flop
- selection of clock edge polarity
- selection of preset and clear for the register
- selection of the true or complement of an output



J.J. Shann 7-86


86

## B. CPLD

### ■ Complex PLD:

- A collection of individual **PLDs** on a single integrated ckt
- Has a **programmable interconnection structure** that allows the PLDs to be connected to each other.

### ■ General CPLD configuration:

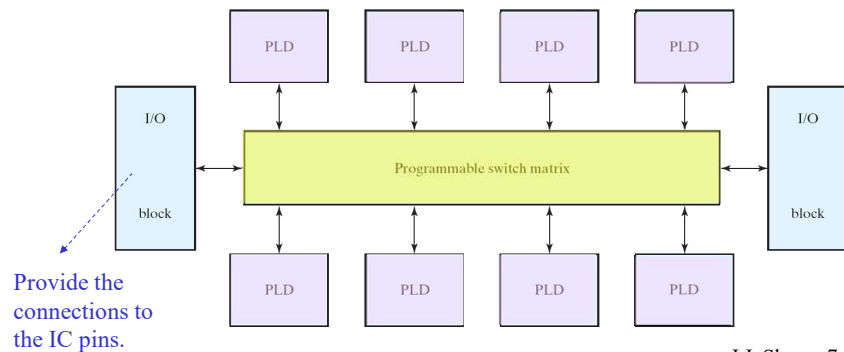

J.J. Shann 7-87

87

## C. FPGA

### ■ Field programmable gate array:

- is a VLSI ckt that can be programmed in the user's location.
- consists of an array of hundreds or thousands of **logic blocks**, surrounded by **programmable input and output blocks** and connected together via **programmable interconnections**.
  - An FPGA logic block:
    - consists of **look-up tables (LUTs)**, **multiplexers**, **gates**, and **flip-flops**.


J.J. Shann 7-88

88

# Xilinx FPGA
 
## Basic Xilinx Architecture:

- consists of
  - an array of **configurable logic blocks (CLBs)**
  - a variety of local and global **routing resources**
  - **input-output blocks (IOBs)**
  - programmable I/O buffers
  - a SRAM-based configuration memory
- E.g.: Xilinx Spartan



J.J. Shann 7-89

89

## Configurable logic block (CLB)


### CLB:

- consists of a programmable lookup table, multiplexers, registers, and paths for control signals

3 LUTs:

F: 4-input LUT  
G: 4-input LUT  
H: 3-input LUT

2 storage devices

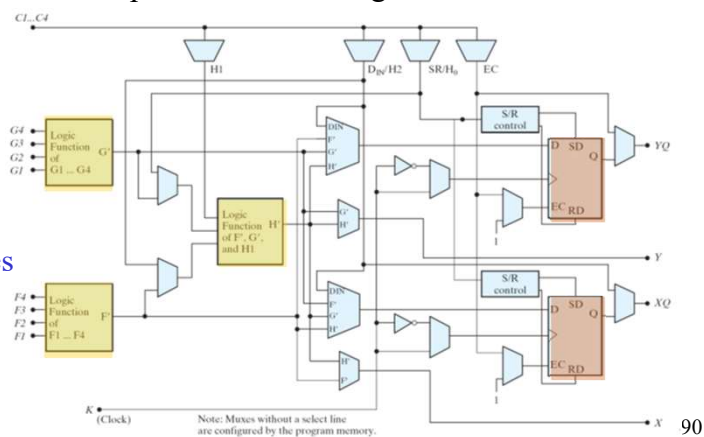


90

90

## Distributed RAM
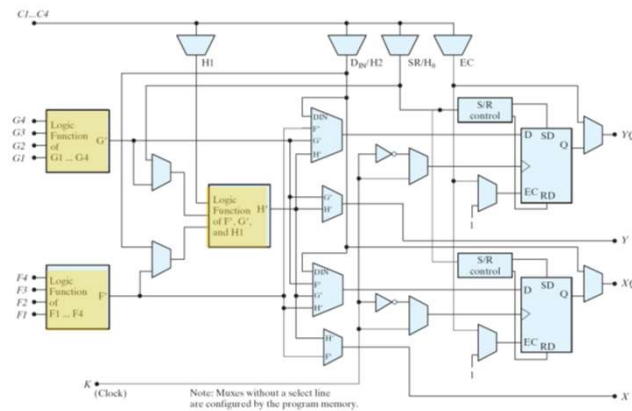
### ■ Distributed RAM:

- The three function generators within a CLB can be used as either a 16×2 dual-port RAM or a 32 × 1 single-port RAM.




91

91

## Interconnect Resources
 
### ■ Interconnect resources:

- a grid of switch matrices
- 3 types of general-purpose interconnects:
  - single-length lines
  - double-length lines
  - long lines



J.J. Shann 7-92

92





## Chapter Summary

---

- Programmable Logic Devices (PLDs):

- Read Only Memory (ROM)
- Programmable Logic Array (PLA)
- Programmable Array Logic (PAL)

- Memory:

- Random Access Memory (RAM): static vs. dynamic
- Memory decoding: linear vs. coincident

J.J. Shann 7-93