



4-12 ~ 4-15

HDL Models of Comb Ckts

Behavioral Modeling

Writing a Simple Testbench

Logic Simulation

J.J. Shann

■34



HDL Models of Combinational Ckts

* 1 module per file (.v) w/ the same name

■ Module:

- the basic building block for modeling hardware w/ the Verilog HDL

■ Modeling styles of a module:

- **gate-level** modeling: use instantiations of *predefined* and *user-defined primitive gates*
 - describes a ckt by specifying its **gates** and how they are connected w/ each other
- **dataflow** modeling: use *continuous assignment statements* w/ the keyword **assign**
 - is used mostly for describing the **Boolean equations** of **combinational** logic
- **behavioral** modeling: use *procedural assignment statements* w/ the keyword **always**
 - is used to describe **combinational** and **sequential** ckts at a higher level of abstraction


J.J. Shann HDL-35

■35

Verilog Model for Combinational Logic

Figure 4.32

 Relationship of Verilog constructs to truth tables, Boolean equations, and schematics



J.J. Shann HDL-36

■36

A. Gate-Level Modeling

* The output(s) of a primitive is always listed first in the port list, followed by the inputs.

■ Gate-level modeling:

- Provides a texture description of a *schematic diagram*.
 - A ckt is specified by its *logic gates* and their *interconnections*.

■ Predefined primitives of *gates* in Verilog: 12

- 8 digital logic primitive gates:

and, nand, or, nor, xor, nxor, not, buf

n-input 1-output primitives
(can have any # of scalar inputs)

1-input *n*-output primitives
(can drive multiple output lines)

- 4 three-state type primitive gates: p.HDL-47

bufif1, bufif0, notif1, notif0

* The logic of each gate is based on a 4-valued system:

0, 1, x (unknown), z (high impedance)

HDL-37

■37

4-Valued System

- 0
- 1
- *x*: *unknown*
 - An unknown value is assigned during simulation when the *logic value of a signal is ambiguous* (can not be determined whether its value is 0 or 1).
- *z*: *high impedance*
 - occurs at the *output of three-state gates that are not enabled* or if *a wire is inadvertently left unconnected*.
- E.g.: 4-valued logic truth tables (p.208, Table 4.9)

J.J. Shann HDL-38

■38

4-Valued Logic Truth Tables

- E.g.: 4-valued logic truth tables (p.208, Table 4.9)

Truth Table for Predefined Primitive Gates

and	0	1
0	0	0
1	0	1

or	0	1
0	0	1
1	1	1

xor	0	1
0	0	1
1	1	0

not	input	output
	0	1
	1	0


39

■39

HDL Example 4.1: 2-to-4 Line Decoder

■ HDL Example 4.1: 2-to-4 Line Decoder

- *gate-level* description of Fig 4.19

 

```

module decoder_2x4_gates (D, A, B, enable);
  output [0:3] D;
  input      A, B;
  input      enable;
  wire       A_not, B_not, enable_not;

  not
    G1 (A_not, A),
    G2 (B_not, B),
    G3 (enable_not, enable);

  nand
    G4 (D[0], A_not, B_not, enable_not),
    G5 (D[1], A_not, B, enable_not),
    G6 (D[2], A, B_not, enable_not),
    G7 (D[3], A, B, enable_not);

endmodule

```

The keyword “not” may be written only once for the three gates.

■40

■ *vector*:

- a multiple-bit width identifier
- e.g.s:

```

output [0:3] D;
wire    [7:0] SUM;

```

- includes within “[]” 2 numbers separated w/ a “:”
 - The 1st number listed is always the MSB of the vector.
 - The individual bits are specified within [], D[2].
 - may address parts (contiguous bits) of vectors, SUM[2: 0].

■ *wire*: for internal connections

- * The output is always listed first in the port list of a primitive, followed by the inputs.

```

module decoder_2x4_gates (D, A, B, enable);
  output [0:3] D;
  input      A, B;
  input      enable;
  wire       A_not, B_not, enable_not;

  not
    G1 (A_not, A),
    G2 (B_not, B),
    G3 (enable_not, enable);

  nand
    G4 (D[0], A_not, B_not, enable_not),
    G5 (D[1], A_not, B, enable_not),
    G6 (D[2], A, B_not, enable_not),
    G7 (D[3], A, B, enable_not);

endmodule

```

J.J. Shann HDL-41

■41

Design Methodologies of Digital Circuits

■ 2 basic design methodologies: *hierarchical*

- **bottom-up** design: the building blocks are first identified and then combined to build the top-level block

➤ E.g.:

Half adder (HA): add two bits, 1 XOR gate + 1 AND gate

⇒ Full adder (FA): add three bits, 2 HAs + 1 OR gate

⇒ n -bit ripple-carry adder (RCA): add 2 n -bit numbers, n FAs

- **top-down** design: the top-level block is defined and then the subblocks necessary to build the top-level block are identified

➤ E.g.:

n -bit ripple-carry adder (RCA) ⇒ n full adders (FAs)

Full adder ⇒ 2 half adders (HAs) + 1 OR gate

Half adder ⇒ 1 XOR gate + 1 AND gate

J.J. Shann HDL-42

■42

HDL Example 4.2: Ripple-Carry Adder


■ HDL Example 4.2: 4-bit Ripple-Carry Adder

- *gate-level* description

- *bottom-up*
hierarchical
description:

HA → FA → RCA

- HA: Fig 4.5(b)

 

// Description of half adder


```
// module half_adder (S, C, x, y);
//   output  S, C;
//   input   x, y;
```

// Alternative Verilog 2005 syntax:

```
module half_adder (output S, C, input x, y);
// Instantiate primitive gates
  xor (S, x, y);
  and (C, x, y);
endmodule
```

J.J. Shann HDL-43

■43

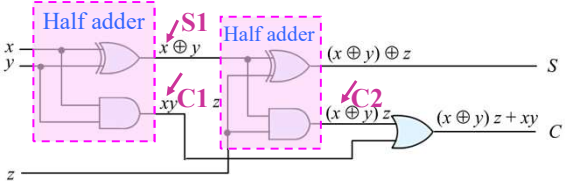

— FA: Fig 4.8

HA module

```

module half_adder (output S, C,
                  input x, y);
    xor (S, x, y);
    and (C, x, y);
endmodule

```

```


// Description of full adder
// module full_adder (S, C, x, y, z);
// output S, C;
// input x, y, z;

// alternative Verilog 2005 syntax:
module full_adder (output S, C, input x, y, z);
    wire S1, C1, C2;

    // Instantiate half adders
    half_adder HA1 (S1, C1, x, y);
    half_adder HA2 (S, C2, S1, z);
    or G1 (C, C2, C1);
endmodule

```

■44

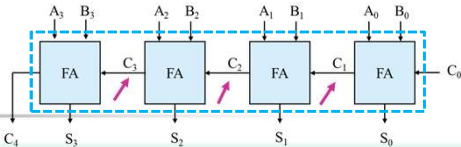

— 4-bit RCA:
Fig 4.9

```

// Description of 4-bit adder (see Fig 4-9)
// module ripple_carry_4_bit_adder (Sum, C4, A, B, C0);
// output [3:0] Sum;
// output C4;
// input [3:0] A, B;
// input C0;

// Alternative Verilog 2005 syntax:
module ripple_carry_4_bit_adder ( output [3:0] Sum,
    output C4, input [3:0] A, B, input C0);
    wire C1, C2, C3; // Intermediate carries

    // Instantiate chain of full adders
    full_adder FA0 (Sum[0], C1, A[0], B[0], C0),
    FA1 (Sum[1], C2, A[1], B[1], C1),
    FA2 (Sum[2], C3, A[2], B[2], C2),
    FA3 (Sum[3], C4, A[3], B[3], C3);
endmodule

```

FA module

```

module full_adder (output S, C,
                  input x, y, z);
    wire S1, C1, C2;
    half_adder HA1 (S1, C1, x, y);
    half_adder HA2 (S, C2, S1, z);
    or G1 (C, C2, C1);
endmodule

```

■45

■ Module declarations **cannot** be *nested*.

- A module definition (declaration) cannot be placed within another module declaration.

⇒ A module definition **cannot** be inserted into the text b/t the **module** and **endmodule** keywords of another module.

■ Modules can be instantiated within other modules.

- Creates a *hierarchical* decomposition of a design.
⇒ *structural* description

* One module per file (.v) & w/ the same name.

J.J. Shann HDL-46

■46



Three-State Gates

■ Three-state gate:



- has a **control input** that can place the gate into a *high-impedance* state (**z**).

■ Types of three-state gates: 4

- **bufif1**
- **bufif0**

  

- **notif1**
- **notif0**

  


J.J. Shann HDL-47

■47

■ Three-state gates:

- **bufif1, bufif0,**
notif1, notif0

 

- are instantiated w/ the statement
gate name (output, input, control);
- In simulation, the output can result in 0, 1, x, or z.
- The outputs of 3-state gates can be connected together to form a common output line.

J.J. Shann HDL-48


■48

HDL Example: 2-to-1 Line Multiplexer

■ HDL Example: 2-to-1 Line MUX w/ three-state buffers

- p.205, Fig 4.30
- **tri**: for tristate
 - indicate that the output has multiple drivers
- Types of 3-state gates:
bufif1, bufif0, notif1, notif0
- Instantiate of a 3-state gate:


gate name (output, input, control);

 

```
module mux_tri (m_out, A, B, select);
    output m_out;
    input  A, B, select;
    tri   m_out;
    bufif1 (m_out, A, select);
    bufif0 (m_out, B, select);
endmodule
```

J.J. Shann HDL-49

■49




- **nets**: a class of data types
 - represent connections b/t hardware elements
 - e.g.s: **wire**, **wor**, **wand**, **tri**, **supply1**, **supply0**

```

graph TD
    A[wired-OR] --> B[wire]
    C[wired-AND] --> D[wand]
    E[power supply (1)] --> F[supply1]
    G[ground (0)] --> H[supply0]
          
```
 - If an identifier is used, but not declared, the language specifies that it will be interpreted (by default) as a **wire**.

J.J. Shann HDL-50

■50



B. Dataflow Modeling

- **Dataflow modeling**:
 - uses a number of operators that act on binary operands to produce a binary result.
 - Commonly used Verilog HDL operators: p.222, Table 4.10

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!

J.J. Shann HDL-51

■51

■ Commonly used Verilog HDL operators: Table 4.10

Symbol	Operation	Symbol	Operation
+	binary addition		
−	binary subtraction		
&	bitwise AND	&&	logical AND
	bitwise OR		logical OR
^	bitwise XOR		
~	bitwise NOT	!	logical NOT
==	equality		
>	greater than		
<	less than		
{}	concatenation		
?:	conditional		

J.J. Shann HDL-52

■52

Symbol	Operation	Symbol	Operation
+	binary addition		
−	binary subtraction		
&	bitwise AND	&&	logical AND
	bitwise OR		logical OR
^	bitwise XOR		
~	bitwise NOT	!	logical NOT
==	equality		
>	greater than		
<	less than		
{}	concatenation		
?:	conditional		

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!

– *bitwise* operators: operate bit by bit on a pair of **vector operands** to produce a **vector result**

➤ E.g.: ~(1010) is (0101)

– *logical* operators:

➤ E.g.: !(1010) is 0

* If the operands are *scalar*, the results of *bitwise* and *logical* operators will be identical; if the operands are **vectors**, the result will not necessarily match.

– *concatenation* operator: {}, append multiple operands

– *conditional* operator: ?:, acts like a multiplexer

condition ? true-expression : false-expression

J.J. Shann HDL-53

■53

* If the operands are scalar, the results will be identical; if the operands are vectors, the result will not necessarily match.

■ Example: $A = 1010$, $B = 0000$

- A has the Boolean value 1, B has Boolean value 0.
- Results of other operations with these values:

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!


■57

Dataflow Modeling of Comb. Logic

■ Dataflow modeling of combinational logic:

- Describes combinational ckts by their *function* rather than by their gate structure
- uses *continuous assignments* and the keyword **assign**.
- E.g.: a 2-to-1-line MUX w/ scalar data inputs A and B , select input S , and output Y

assign $Y = (A \&\& S) || (B \&\& !S);$

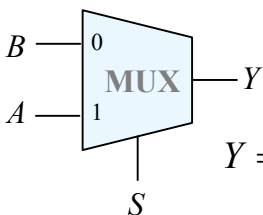

$$Y = SA + \bar{S}B$$

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!


J.J. Shann HDL-58

■58

HDL Example 4.3: 2-to-4 Line Decoder (Dataflow)

■ HDL Example 4.3: (Dataflow)

– *dataflow* description of Fig 4.19

 

	Bitwise	Logical
AND	&	&&
OR		
NOT	~	!

//Verilog 2001, 2005 Syntax

```
module decoder_2x4_df (
    output [0:3] D,
    input A, B,
    input enable
);
```

$D_0 = (A' B' E)'$

$D_1 = (A' B E)'$

$D_2 = (A B' E)'$

$D_3 = (A B E)'$

```
assign D[0] = !((!A) && (!B) && (!enable)),
       D[1] = !((!A) && B && (!enable)),
       D[2] = !(A && (!B) && (!enable)),
       D[3] = !(A && B && (!enable));
```


endmodule

■59

HDL Example 4.4: 4-bit Adder (Dataflow)

■ HDL Example 4.4: (Dataflow) 4-bit adder

– *dataflow* description of 4-bit adder

 

// Verilog 2005 module port syntax

```
module binary_adder (
    output [3:0] Sum,
    output C_out,
    input [3:0] A, B,
    input C_in
);
```

```
assign {C_out, Sum} = A + B + C_in;
endmodule
```

5-bit result of the addition operation


J.J. Shann HDL-60

■60

Symbol	Operation	Symbol	Operation
+	binary addition	&&	logical AND
-	binary subtraction		logical OR
&	bitwise AND	!	logical NOT
	bitwise OR		
^	bitwise XOR		
~	bitwise NOT		
==	equality		
>	greater than		
<	less than		
{ }	concatenation		
?:	conditional		

HDL Example 4.5: 4-bit Comparator (Dataflow)

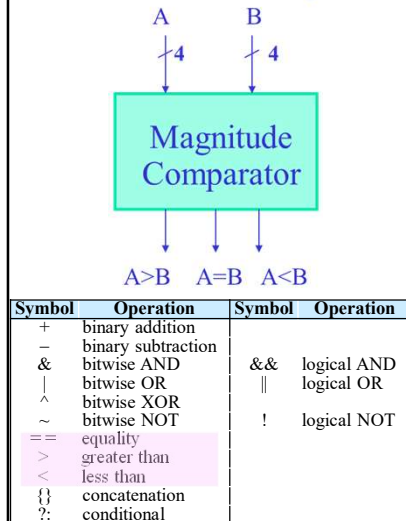HDL Example 4.5: (Dataflow) 4-bit comparator



```
// Verilog 2001, 2005 syntax
module mag_compare (
    output A_lt_B, A_eq_B, A_gt_B,
    input  [3:0] A, B
);


    assign A_lt_B = (A < B);
    assign A_gt_B = (A > B);
    assign A_eq_B = (A == B);
endmodule
```

J.J. Shann HDL-61

■61

HDL Example 4.6: 2-to-1 MUX (Dataflow)

HDL Example 4.6: (Dataflow) 2-to-1 MUX

 

```
// Verilog 2001, 2005 syntax
module mux_2x1_df(m_out, A, B, select);
    output m_out;
    input  A, B;
    input  select;

    assign m_out = (select)? A : B;
endmodule
```

– *conditional* operator: **?:**
condition ? true-expression : false-expression

J.J. Shann HDL-62

■62

C. Behavioral Modeling

* **reg** data type:
retains its value until a
new value is assigned

■ Behavioral modeling:

- represents digital ckts at a *functional* and *algorithmic* level
- is used mostly to describe *sequential* ckts, but can also be used to describe *combinational* ckts.
- use keyword **always**, followed by an optional *event control expression* and a list of *procedural assignment statements*.

```
always @ (event control expression) begin  
    //procedural assignment statements
```

end specifies when the statements will execute

- The procedural assignment statements inside the **always** block are executed every time there is a change in *any* of the variables listed after the @ symbol. separated by keyword **or** or **“,”**

* The target output of the procedural assignment statement must be **reg** data type.

J.J. Shann HDL-63

■63

■ if-else conditional statement

■ case statement: **case ... endcase**

- a multiway conditional branch construct
- The case items have an implied priority because the list is evaluated from top to bottom.


J.J. Shann HDL-64

■64

HDL Example 4.7: 2-to-1 MUX (Behavioral)

■ HDL Example 4.7: (Behavioral) 2-to-1 Line MUX

 – Behavioral description of 2-to-1 line MUX



```
// Verilog 2001, 2005 syntax
module mux_2x1_beh(
  output reg m_out,
  input  A, B, select
);

  always @(A or B or select) //@(A, B, select)
    if (select == 1) m_out = A; //(select)
    else m_out = B;
endmodule
```

* The target output of the procedural assignment statement inside always must be reg data type.

* Use blocking assignments (=) in always block for combinational logic.


– if-else conditional statement

■65

HDL Example 4.8: 4-to-1 Line MUX (Behavioral)

■ HDL Example 4.7: (Behavioral) 4-to-1 Line MUX

 – Behavioral description of 4-to-1 line MUX



```
// Verilog 2001, 2005 syntax
module mux_4x1_beh
( output reg m_out,
  input  in_0, in_1, in_2, in_3,
  input [1:0] select
);

  always @(in_0, in_1, in_2, in_3, select)
    case (select)
      2'b00: m_out = in_0;
      2'b01: m_out = in_1;
      2'b10: m_out = in_2;
      2'b11: m_out = in_3;
    endcase
endmodule
```

case items, have implied priority (top to bottom)

■66

case Construct

■ case statement: **case ... endcase**

- a multiway conditional branch construct
- The case items have an implied priority because the list is evaluated from top to bottom.

■ **default**: the last item in the list of **case** items, for unlisted **case** items

■ 2 important variations of **case** construct:

- **casex**: don't-care any bits of the **case** expression or the **case** item that have logic value **x** or **z**
- **casez**: don't-care only the logic value **z**

x: unknown

z: high-impedence

J.J. Shann HDL-67

■67

Numbers

N'Bvalue

size in bits

base

■ Numbers can be specified in *binary*, *octal*, *decimal*, or *hexadecimal* (bases 2, 8, 10, 16):


- Underscores (`_`) in numbers are ignored and can be helpful in breaking long numbers into more readable chunks.

■ Format for declaring constants: **N'Bvalue**

- **N**: the size in bits, leading zeros are inserted to reach this size
 - optional, but better give the size explicitly.
 - If the size is not specified, the system assumes that it is the word length of the host simulator or at least 32 bits.
- **B**: the letter indicating the base
 - **'b** for *binary*, **'o** for *octal*, **'d** for *decimal*, and **'h** for *hexadecimal*
 - If the base is omitted, it defaults to *decimal*.
- **value**: gives the value

J.J. Shann 1-68

■68



N'Bvalue

size in bits

base


■ Examples: Harris, Table 4.3, p.180

Numbers	Bits	Base	Val	Stored
3'b101				
'b11				
8'b11				
8'b1010_1011				
3'd6				
6'o42				
8'hAB				
42				

* '0, '1: fill a bus w/ all 0s and all 1s

J.J. Shann 1-69

■69



Summary

■ Guidelines of modeling *combinational* logic:

- Gate-level modeling
- Dataflow modeling:

assign y = s ? d1 : d2;

 - Use *continuous assignments* **assign** to model *simple combinational* logic.
- Behavioral modeling:


```

always @ (*)
begin
  p = a ^ b; //blocking
  q = a & b; //blocking
  s = p ^ cin;
  cout = q | (p & cin);
end
          
```

 - Use **always @ (*)** and *blocking assignments* to model more *complicated combinational* logic where the **always** statement is helpful.

* Do not make assignments to the same signal in more than one **always** statement or continuous assignment statement.


J.J. Shann HDL-70

■70

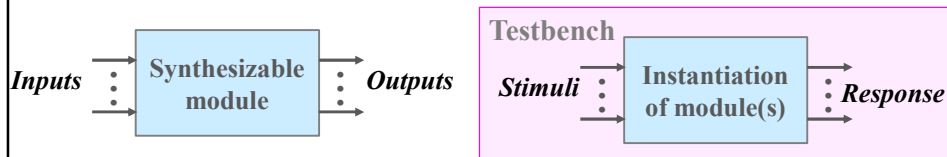D. Writing a Simple Test Bench

■ Test bench:

- is an HDL program used for describing and applying a *stimulus* to an HDL model of a ckt in order to test it and observe its *response* during *simulation*.
- Write stimuli that will test a ckt thoroughly, exercising all of the operating features that are specified.
- can be complex and lengthy and may take longer to develop than the design that is tested.
- The results of a test are only as good as the test bench that is used to test a ckt.



■71

(a) Providing Input Stimulus

■ Statements used by a test bench to provide a stimulus to the ckt being tested:

- **initial** statement: *executes only once*
 - starting from *simulation time 0*, and may continue w/ any operations that are delayed by a given number of time units, as specified by the symbol **#**.
- **always** statement: *executes repeatedly in a loop*
 - specify how the associated statement is to execute (the *event control expression*)

```
always @ (event control expression) begin
    //procedural assignment statements
end
```

J.J. Shann HDL-72

■72

■ **Example:**

stimulus	A	B
(t = 0)	0	0
(t = 10)	1	0
(t = 30)	0	1

■ **Example:**

stimulus	D
(t = 0)	000
(t = 10)	001
...	
(t = 70)	111

– **repeat:** specifies a looping statement

Initial

begin

A = 0; B = 0;

#10 A = 1;

#20 A = 0; B = 1;

end

Initial

begin

D = 3'b000;

repeat (7)

#10 D = D + 3'b001;


end

J.J. Shann HDL-73

■73

■ **Example:**

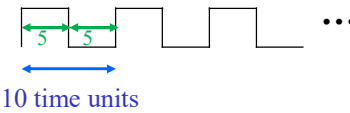generate periodic clock pulse (period = 10 time units)



always

begin

clock = 1; #5; clock = 0; #5;

end

J.J. Shann HDL-74

■74



(b) Displaying Output Response to the Stimulus

- The response of the stimulus generated by the **initial** and **always** blocks will appear:
 - in **text format** as standard output &
 - as **waveforms** (**timing diagrams**) in simulators having graphical output capability
- Numerical outputs are displayed by using Verilog ***system tasks***.
- Verilog system tasks:
 - are built-in system functions that are recognized by keywords that begin with the symbol **\$**.

J.J. Shann HDL-75

■75



System Tasks for Display

- **\$display**: display a one-time value of variables or strings with an end-of-line return
- **\$write**: same as **\$display**, but w/o going to next line
- **\$monitor**: display variables whenever a value changes during a simulation run
- **\$time**: display the *simulation time*
- **\$finish**: terminate the simulation

- Syntax for **\$display**, **\$write**, and **\$monitor**:
(next page)

J.J. Shann HDL-76

■76

■ Syntax for \$display, \$write, and \$monitor:

Task-name (format specification, argumentlist);

– format specification:

- uses the symbol % to specify the radix of the numbers that are displayed : %b, %d, %h, %o (%B, %D, %H, %O)
- may have a string enclosed in quotes (".....")
- No commas in the format specification.

– argument list:

- has commas b/t the variables.

– E.g.s:

\$display ("%d %b %b", C, A, B);

\$display ("time = %0d A = %b B = %b", \$time, A, B);

format specification

argument list

J.J. Shann HDL-77



%d: w/ the leading spaces

%0d: w/o the leading spaces

* In displaying time values, use the format %0d instead of %d.
(Time is calculated as a 32-bit number.)

■77

(c) Testbench

  


■ Form of a test bench:

```
module test_module_name;    //no port list
//Declare local reg and wire identifiers.
//Instantiate the design module(s) under test.
//Specify a stopwatch, using $finish to terminate the simulation.
//Generate stimulus, using initial and always statements.
//Display the output response (text or graphics, or both).
endmodule
```


- has no inputs or outputs ⇒ No port list!
- The signals that are applied as inputs to the design module for simulation are declared in the stimulus module as local reg data type.
- The outputs of the design module that are displayed for testing are declared in the stimulus module as local wire data type.

J.J. Shann HDL-78


■78

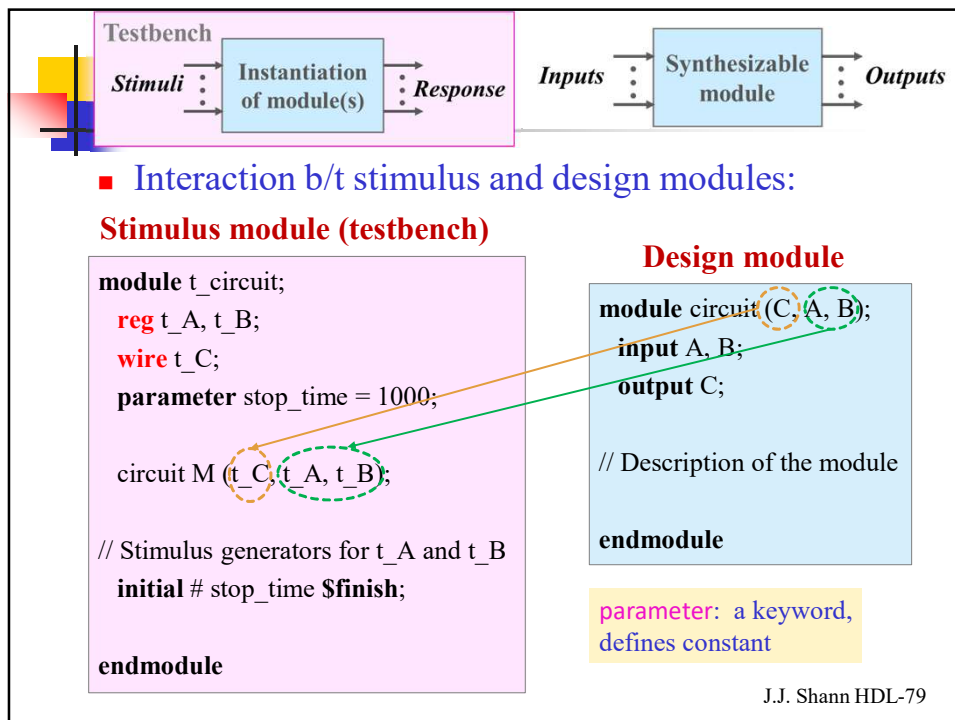

■79

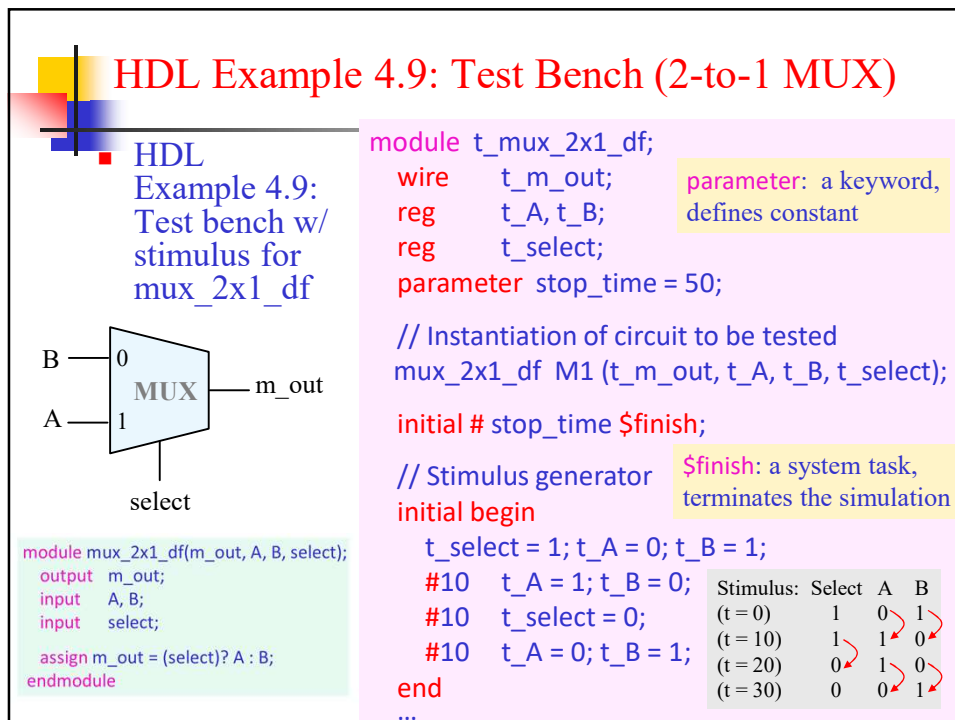

■80

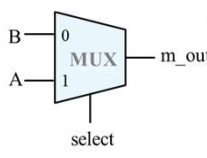

```

module mux_2x1_df(m_out, A, B, select);
  output m_out;
  input A, B;
  input select;
  assign m_out = (select)? A : B;
endmodule

```

Simulation log:

Select = 1	A = 0	B = 1	OUT = 0	time = 0
Select = 1	A = 1	B = 0	OUT = 1	time = 10
Select = 0	A = 1	B = 0	OUT = 0	time = 20
Select = 0	A = 0	B = 1	OUT = 1	time = 30

```

module t_mux_2x1_df;
  //Declaration of local identifiers
  ...
  // Instantiation of circuit to be tested
  ...
  // Stimulus generator
  ...
  //Response monitor
  initial begin
    $display("   time  Select A   B   m_out");
    $monitor($time, " %b  %b  %b  %b", t_select, t_A, t_B, t_m_out);
    //$monitor("time=", $time, "select = %b A = %b B = %b m_out = %b",
    t_select, t_A, t_B, t_m_out);
  end
endmodule

```

\$display: a system task,
print in the simulator
window

\$monitor: a system task,
displays the output
caused by the given
stimulus


■81

HDL Example: Design Module & Test Bench

(1/2)

■ HDL Example:
Design Module &
Test bench of Fig 4.2

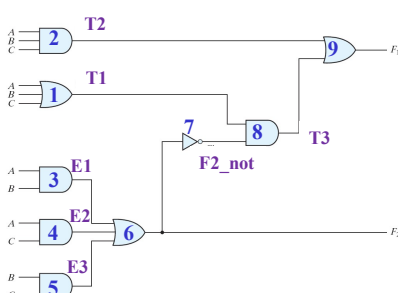— *gate-level* description
of ckt of Fig 4.2



```

module Circuit_of_Fig_4_2 (
  output F1, F2,
  input A, B, C);
  wire T1, T2, T3, F2_not, E1, E2, E3;

  or G1 (T1, A, B, C);
  and G2 (T2, A, B, C);
  and G3 (E1, A, B);
  and G4 (E2, A, C);
  and G5 (E3, B, C);
  or G6 (F2, E1, E2, E3);
  not G7 (F2_not, F2);
  and G8 (T3, T1, F2_not);
  or G9 (F1, T2, T3);
endmodule


```

■82

HDL Example: Design Module & Testbench

(2/2)

- Stimulus to analyze the ckt of Fig 4.2

 

```

module Circuit_of_Fig_4_2 (
    output F1, F2,
    input  A, B, C;
    wire   T1, T2, T3, F2_not, E1, E2, E3;

    or  G1 (T1, A, B, C);
    and G2 (T2, A, B, C);
    and G3 (E1, A, B);
    and G4 (E2, A, C);
    and G5 (E3, B, C);
    or  G6 (F2, E1, E2, E3);
    not G7 (F2_not, F2);
    and G8 (T3, T1, F2_not);
    or  G9 (F1, T2, T3);
endmodule
  
```

```

module t_Circuit_of_Fig_4_2;
    reg [2:0] D; //A, B, C
    wire F1, F2;
    parameter stop_time = 100;
  
```

```

    Circuit_of_Fig_4_2 M1 (F1, F2, D[2], D[1], D[0]);
  
```

```

    initial # stop_time $finish;
  
```

```

    initial begin // Stimulus generator
        D = 3'b000;
    
```

```

        repeat (7) #10 D = D + 1'b1;
    
```

```

    end
  
```

```

    initial begin //Response monitor
    
```

```

        $display("A B C F1 F2");
    
```

```

        $monitor("%b %b %b %b %b", D[2],
            D[1], D[0], F1, F2);
    
```

```

    end
  
```

```

endmodule
  
```

Simulation log:

```

ABC = 000 F1 = 0 F2 = 0
ABC = 001 F1 = 1 F2 = 0
ABC = 010 F1 = 1 F2 = 0
ABC = 011 F1 = 0 F2 = 1
ABC = 100 F1 = 1 F2 = 0
ABC = 101 F1 = 0 F2 = 1
ABC = 110 F1 = 0 F2 = 1
ABC = 111 F1 = 1 F2 = 1
  
```