



Chapter 6

Registers and Counters

J.J. Shann


1



§6-2

1. Given the function table of a 2-bit shift register, derive the input equation for each D flip-flop of the register and draw the logic diagram of the register.

CLK	S_1	S_0	A_1^+	A_0^+	Register Operation
↓	0	0	A_1	A_0	No Change
↓	0	1	I_1	I_0	Parallel load
↓	1	0	A_0	SI	Shift left

 


EX-2

2



§6-3

2. Given the counting sequence of a 2-bit binary counter, design a **ripple** counter using negative-edge triggered D flip-flops. Derive and draw your logic circuit.

Q_1	Q_0
1	1
1	0
0	1
0	0

 

<Ans>

  


EX-3

3



§6-4

3. Given the counting sequence of a 2-bit binary counter, design a **synchronous** counter using D flip-flops. Derive the flip-flop input equations and draw the logic diagram of the circuit.

Q_1	Q_0
1	1
1	0
0	1
0	0

 

<Ans>

  

EX-4


4



§6-4

4. Given the function table and the block diagram of a 4-bit binary up-counter, implement a counter that follows the sequence 0101 through 1011 and then repeats using the *load* input.

Clear	CLK	Load	Count	Function
0	x	x	x	Clear to 0
1	↑	1	x	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

 

EX-5

5



Brief Answers of the Exercises

1. $D_1 = S_1'S_0'A_1 + S_1'S_0I_1 + S_1S_0'A_0$, $D_0 = S_1'S_0'A_0 + S_1'S_0I_0 + S_1S_0'SI$

2. $FF_0: C_0: \text{CLOCK}, D_0 = Q_0'$
 $FF_1: C_1: Q_0 \uparrow \Rightarrow Q_0' \downarrow, D_1 = Q_1'$

3. $D_1 = Q_1^+ = Q_1 \oplus Q_0'$, $D_0 = Q_0^+ = Q_0'$

EX-6

6