



Chapter 5

Synchronous Sequential Logic


J.J. Shann

1



§5-3

 1. Given two cross-couple NAND gates, assume that the propagation delay (*PD*) of each gate is 10 ns. Draw the timing waveform for outputs C and D, and estimate the time required for the outputs to become stable in the following conditions:



(a) $A = 1, B = 0, C = 1,$ and $D = 0$


- (b) i. $A = 0, B = 1, C = 0,$ and $D = 1$
ii. $A = 0, B = 0, C = 0,$ and $D = 1$
iii. $A = 1, B = 1, C = 1,$ and $D = 1$

EX-2

2

§5-4

 2. Given the following logic diagram, explain why it is a negative-edge-triggered D flip-flop.




EX-3


3

<Ans>


i. When clock is HIGH:

 

ii. When clock goes HIGH-to-LOW:

 

 iii. When clock is LOW and D is changed to D' :



EX-4

4



§5-5

3. A synchronous sequential circuit with two D flip-flops A and B , two inputs X and Y , and one output Z is specified by the following equations:

$$D_A = \bar{X}A + XY$$

$$D_B = \bar{X}A + XB$$

$$Z = A\bar{B}$$

- Draw the logic diagram of the circuit.
- Derive the next state equations.
- Complete the transition/state table of the circuit.
- Draw the state diagram.
- Starting from state 00 in the state diagram, determine the state transitions and output sequence that will be generated when an input sequence of $XY = 01, 11, 11, 00, 10, 01, 11, 10$ is applied.

EX-5


5

<Ans>

Transition/state table:

Present state		Input		Next state		Output
A	B	X	Y	A+	B+	Z
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

State diagram:

 


Cycle	0	1	2	3	4	5	6	7	8
xy	01	11	11	00	10	01	11	10	
AB	00								
Z									

EX-6

6

§5-5

 4. Analyze the following synchronous sequential circuit, which has one input x and one output z , step by step:



- Derive the memory input equations and the output equation.
- Derive the next state equations.
- Complete the transition/state table of the circuit.
- Draw the state diagram.

EX-7


7

<Ans>

Transition/state table:

Present state		Input	Next state		Output
A	B	X	A+	B+	Z
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

State diagram:

 


EX-8

8

補充資料：Sync Seq Ckt Timing

 5. A sequential circuit is given in the following figure. The timing parameters for the gates and flip-flops are as follows:

Inverter: $t_{pd} = 0.5$ ns
 XOR Gate: $t_{pd} = 2.0$ ns
 Flip-flop: $t_{pd} = 2.0$ ns,
 $t_s = 1.0$ ns, and
 $t_h = 0.25$ ns




- Find the longest path delay from an external circuit input passing through gates only to an external circuit output.
- Find the longest path delay in the circuit from an external input to positive clock edge.
- Find the longest path delay from positive clock edge to output.
- Find the longest path delay from positive clock edge to positive clock edge.
- Determine the maximum frequency of operation of the circuit in megahertz (MHz).


EX-9

9

 
- (a) external circuit input \rightarrow external circuit output:



 
- (b) external input \rightarrow positive clock edge:



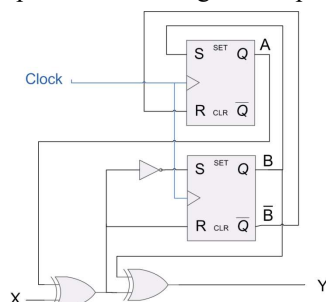- (c) positive clock edge \rightarrow output:



 - (d) positive clock edge \rightarrow positive clock edge:



EX-10

10

§5-7 & 5-8

6. Design a Moore-type recognizer which has one input (X) and one output (Z). The output is asserted (= 1) whenever the input sequence ...010... has been observed, as long as the sequence ...100... has not been seen since the last reset.
- (a) Draw the state diagram of the recognizer.
- (b) Starting from the initial state of your design, determine the state transitions and output sequence that will be generated when an input sequence of 00111010100101 is applied.

<Ans>


Cycle	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Input	0	0	1	1	1	0	1	0	1	0	0	1	0	1	
State	A														
Output															

11

補充資料：State Reduction

7. Given the following state table,
- (a) Use the row matching method to find the equivalent states.
- (b) Use the implication chart method to find the equivalent states. Tabulate the reduced state table.

Present state	Next state		Output	
	x = 0	x = 1	x = 0	x = 1
S ₀	S ₁	S ₄	0	0
S ₁	S ₁	S ₂	0	0
S ₂	S ₁	S ₆	0	0
S ₃	S ₁	S ₃	0	0
S ₄	S ₅	S ₄	0	0
S ₅	S ₅	S ₂	0	0
S ₆	S ₅	S ₃	0	1

 

EX-12

12

§5-7 & 5-8

9. Given the following state (transition) table, treat the unused state as don't-care conditions.

Implement the circuit with **D** flip-flops. Derive the minimized Boolean equations in sum-of-products form for the flip-flop inputs and the output **Z**.

Present state		Input	Next state		Output
Q_A	Q_B	X	Q_{A+}	Q_{B+}	Z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	0	1	0

<Ans>

A	Bx			
	00	01	11	10
0				
1				

A	Bx			
	00	01	11	10
0				
1				

A	Bx			
	00	01	11	10
0				
1				

EX-14

14

§5-7 & 5-8

10. Given the following state (transition) table, treat the unused state as don't-care conditions.

Implement the circuit with **JK** flip-flops. Complete the excitation table shown above and derive the minimized Boolean equations in sum-of-products form for the flip-flop inputs.

Present state		Input	Next state		Output	Excitation Table Flip-Flop Inputs			
Q_A	Q_B	X	Q_{A+}	Q_{B+}	Z	J_A	K_A	J_B	K_B
0	0	0	0	0	0				
0	0	1	0	1	0				
0	1	0	1	0	0				
0	1	1	1	0	1				
1	0	0	0	1	1				
1	0	1	0	1	0				

EX-15

15

<Ans>

Present state		Input	Next state		Output	Excitation Table Flip-Flop Inputs			
Q_A	Q_B	X	Q_{A+}	Q_{B+}	Z	J_A	K_A	J_B	K_B
0	0	0	0	0	0				
0	0	1	0	1	0				
0	1	0	1	0	0				
0	1	1	1	0	1				
1	0	0	0	1	1				
1	0	1	0	1	0				

Bx

A	00	01	11	10
0				
1				

Bx

A	00	01	11	10
0				
1				

Bx

A	00	01	11	10
0				
1				

Bx

A	00	01	11	10
0				
1				

EX-16

16

補充資料：Word Problems

* Give an example of synchronous sequential circuits by yourself. Describe the problem, define the input variables, output variables, and states, and draw the state diagram of the problem.

EX-17

17



Brief Answers of the Exercises

1. (a) C: $1 \rightarrow 1 \rightarrow 0 \rightarrow 0 \rightarrow \dots$, D: $0 \rightarrow 1 \rightarrow 1 \rightarrow 1 \rightarrow \dots$; 20 ns
 (b) i. C: $0 \rightarrow 1 \rightarrow 1 \rightarrow 1 \rightarrow \dots$, D: $1 \rightarrow 1 \rightarrow 0 \rightarrow 0 \rightarrow \dots$; 20 ns
 ii. C: $0 \rightarrow 1 \rightarrow 1 \rightarrow \dots$, D: $1 \rightarrow 1 \rightarrow 1 \rightarrow \dots$; 10 ns
 iii. C: $1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \rightarrow \dots$, D: $1 \rightarrow 0 \rightarrow 1 \rightarrow 0 \rightarrow \dots$; isolated
3. (b) $A(t+1) = x'A + xy$, $B(t+1) = x'A + xB$
 (c) AB: 00 00 10 10 11 01 00 10 00
 Z: 0 0 1 1 0 0 0 1 0
4. (a) $J_A = Bx'$, $K_A = Bx$, $J_B = x$, $K_B = Ax + A'x'$, $Z = Bx'$
 (b) $A^+ = Bx' + AB'$, $B^+ = A'x + B'x + ABx'$
5. (a) 4 ns (b) 3.5 ns (c) 6 ns (d) 5.5 ns (e) 167 MHz
6. (a) 7 states
7. (a) None.
 (b) (0, 3, 4); (1, 5)
9. $D_A = B$, $D_B = A + B'x$, $Z = Bx + Ax'$
10. $J_A = B$, $K_A = 1$, $J_B = A + x$, $K_B = 1$

EX-18